

Code: AC03/AT03 Subject: BASIC ELECTRONICS & DIGITAL CIRCUITS
AMIETE – CS/IT (OLD SCHEME)

Time: 3 Hours

OCTOBER 2012

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated


Q.1 Choose the correct or the best alternative in the following: (2×10)


- a. The measurement of which one of the following will reveal the sign of charge carriers?
- (A) Conductivity (B) Mobility
(C) Hall Coefficient (D) Diffusion Constant
- b. The cascade amplifier is a multistage configuration of
- (A) CC-CB (B) CE-CB
(C) CB-CC (D) CE-CC
- c. The ideal op-amp has the following characteristics
- (A) $R_i=\infty$, $A_i=\infty$, $R_o=0$ (B) $R_i=0$, $A=\infty$, $R_o=0$
(C) $R_i=\infty$, $A=\infty$, $R_o=\infty$ (D) $R_i=0$, $A=\infty$, $R_o=\infty$
- d. Ripple frequency of the output waveform of a bridge rectifier when fed with a 50Hz sine wave is
- (A) 100 Hz (B) 25 Hz
(C) 50 Hz (D) None of these
- e. The sum S of A and B in a half adder can be implemented by using K NAND gates. The value of K is
- (A) 3 (B) 4
(C) 5 (D) None of these

- f. The reason for using Gray Code in K-map is
- (A) gray code is efficient than binary code
 - (B) gray code provides cell values that differ in only one bit in adjacent cell
 - (C) no other code is available
 - (D) Any other code can be used.
- g. The effective channel length of a MOSFET in Saturation decreases with increase in
- (A) Gate Voltage
 - (B) Drain Voltage
 - (C) Source Voltage
 - (D) Base Voltage
- h. Extremely low power dissipation and low cost per gate can be achieved in the following IC
- (A) ECL
 - (B) CMOS
 - (C) TTL
 - (D) MOS
- i. In which flipflop the output is transparent to input?
- (A) JK FF
 - (B) T FF
 - (C) SR FF
 - (D) D FF
- j. Which one of the following statement about RAM is not correct?
- (A) RAM Stands for random access memory
 - (B) It is also called read/write memory
 - (C) When power supply is switched off, the information in RAM is usually lost
 - (D) The binary contents are entered or stored in the RAM chip during the Manufacturing

Answer any FIVE Questions out of EIGHT Questions.

Each question carries 16 marks.

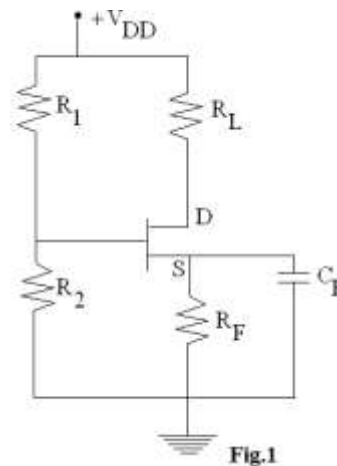- Q.2** a. Explain the input and output characteristics of C B configuration. (8)
- b. A JFET amplifier with stabilized biasing circuit shown in Fig.1 has following parameters:
 $V_P = -2V$, $I_{DSS} = 5mA$, $R_L = 910\Omega$,
 $R_F = 2.29k\Omega$, $R_1 = 12M\Omega$, $R_2 = 8.75M\Omega$
and $V_{DD} = 24V$. Determine the value
of drain current I_D at the operating point.
Also verify that FET will operate in
pinch-off region.
- 




Code: AC03/AT03 Subject: BASIC ELECTRONICS & DIGITAL CIRCUITS

Q.3 a. Derive the general expression for Input impedance, Current gain, Voltage gain and output impedance in terms of h parameter and the load resistance. **(8)**

b. For a BJT $h_{ie} = 500\Omega$, $h_{fe} = 100$, $h_{re} = 10^{-4}$, $h_{oe} = 4 \times 10^{-5} \text{ A/V}$, $V_{CE} = 10\text{V}$, $I_C = 100\text{mA}$ and room temperature of 27°C . The BJT has $f_T = 50\text{MHz}$ and $C_{b'c} = 3\text{pF}$. Calculate all the parameters of the hybrid π model of the BJT. **(8)**

Q.4 a. Explain how LC tank circuit is used to generate AC oscillations in an electronic oscillator? **(8)**

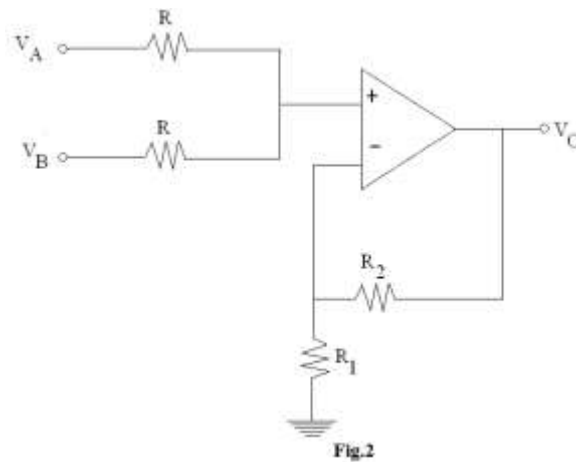b. Find an expression for the output V_o of the amplifier shown in Fig 2. Assume op-amp is ideal. What mathematical operation does this circuit perform? **(8)**



Q.5 a. Explain the working of a full wave bridge rectifier. Explain what is a ripple factor? **(8)**

b. Explain 'Junction diode switching time' to justify diode reverse recovery time. Storage time and transition time. **(8)**

Q.6 a. (i) Write minterms of $A + \overline{B}\overline{C}$
(ii) Write maxterms of $(A+B)(B+C)$ **(4+4)**

b. Explain the operation of a decimal to BCD encoder. **(8)**

Q.7 a. Explain the operation of J-K flip-flop. **(8)**

b. Draw the circuit of a 3 bit synchronous counter and explain its working. **(8)**

Q.8 a. Explain the working of CMOS NAND gate and NOR gate **(8)**

b. Draw a TTL circuit with totem pole output and explain its working **(8)**

Q.9 Write short note on any **TWO** :-**(8×2)**

- (i) CCD
- (ii) Seven segment Display
- (iii) Dynamic MOS
- (iv) Bipolar memory cell.