

AMIETE – ET (OLD SCHEME)

Time: 3 Hours

OCTOBER 2012

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. Which of the following characteristic equation represents a non-linear resistance?

- (A) $v+10i=0$ (B) $i+3v=10$
(C) $v=i^2$ (D) All of these

b. If there are b branches and n nodes, the number of KCL equations required will be

- (A) b (B) n
(C) $(n-1)$ (D) $b-n+1$

c. A 500 watt 220 V bulb is supplied with 110V. The power consumption by the bulb will be _____

- (A) 250 W (B) 125 W
(C) slightly more than 125 W (D) Slightly less than 125 W

d. The Thevenin's impedance between A and B in the circuit shown below in Fig.1 is

- (A) 3.0Ω
(B) 3.75Ω
(C) 3.25Ω
(D) 20Ω

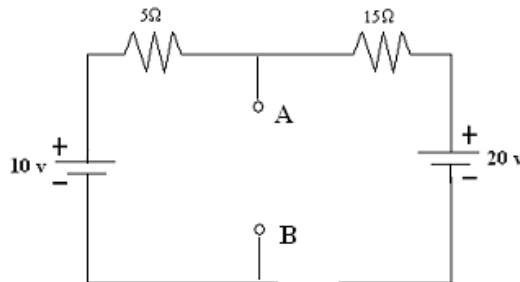


Fig.1

e. What is the efficiency of a network working under maximum power transfer condition?

- (A) 100% (B) 50%
(C) 0.0% (D) 70.7%

- f. In an RLC series circuit, the impedance at resonance is
 (A) minimum (B) maximum
 (C) zero (D) infinity

- g. The open-circuit impedance parameter Z_{11} for the T-network shown below in Fig.2 is

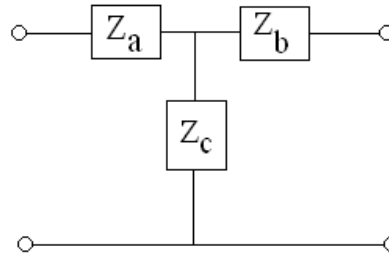


Fig.2

- (A) $Z_a + Z_b$
 (B) $Z_a + Z_b + Z_c$
 (C) $Z_b + Z_c$
 (D) $Z_a + Z_c$
- h. $F(S) = \frac{(S+1)(S+3)}{S(S+2)}$ represents an
 (A) R C impedance
 (B) R C admittance
 (C) R C impedance and an R L admittance
 (D) R L admittance.

- i. The transfer function

$$T(S) = \frac{S^2}{S^2 + aS + b}$$

Belongs to an active

- (A) Low pass filter (B) High pass filter
 (C) Band pass filter (D) Band-reject filter
- j. The coupling between two magnetically coupled coils is said to be ideal if the coefficient of coupling is
 (A) Zero (B) 0.5
 (C) 1 (D) 2

Answer any FIVE Questions out of EIGHT Questions.

Each question carries 16 marks.

- Q.2 a. Explain what do you understand by the duality in reference electrical networks. (8)

- b. Fig.3 shows a network containing one capacitor and several resistors. The capacitor is charged to voltage V_0 . Find the expression for the current $i_1(t)$ through the resistance R_1 .

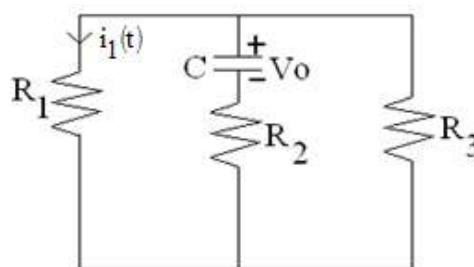


Fig.3

(8)

- Q.3**
- State the superposition theorem in reference to electrical network. Can this theorem be applied directly to calculate the power in an element of the network? Explain. (8)
 - In the network shown below in Fig.4 determine the value of impedance Z_L for maximum power and calculate the maximum power (8)

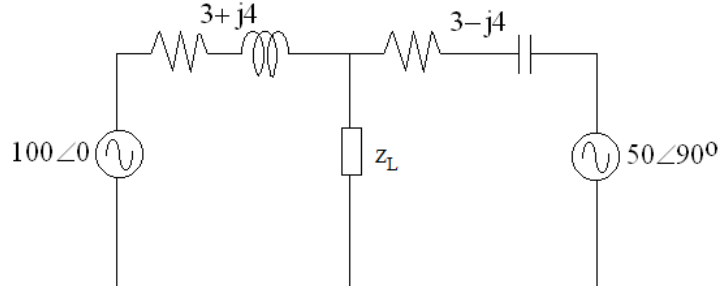


Fig.4

- Q.4**
- Show that the sum of energy stored by the inductor and the capacitor connected in series at resonance at any instant is constant and is given by LI^2 (8)
 - For the circuit shown below in Fig.5
 $Z_1 = (5 - j3)\Omega$, $Z_2 = (4 + j2)\Omega$ and $Z_3 = (2 + j3)\Omega$
 Find:
 (i) The input impedance Z_{in}
 (ii) The input current I
 (iii) The current through Z_2
 (iv) Is the series parallel circuits operating at its resonant frequency? (8)

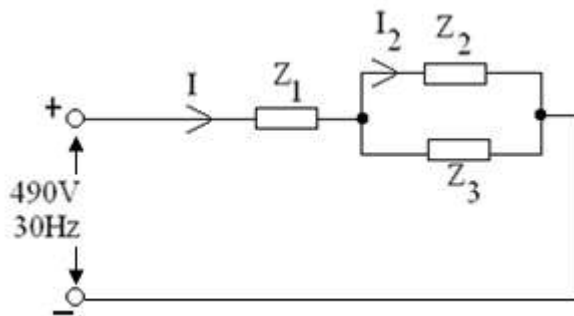


Fig.5

- Q.5**
- Define hybrid-parameters for a two- port network. (8)
 - Obtain Y-parameters of the circuit given below in Fig.6. Draw its equivalent model and find whether the network is reciprocal or symmetrical? (8)

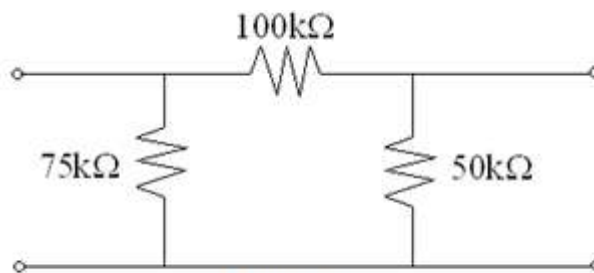


Fig.6

Q.6 a. State the properties of 'POSITIVE REAL FUNCTIONS'. (8)

b. Test whether the polynomial $P(S) = S^5 + 3S^3 + S$ is Hurwitzian or not. (8)

Q.7 a. Synthesize the function $Z(S) = \frac{S(S^2 + 10)}{(S^2 + 4)(S^2 + 16)}$ using first Foster form of realization. (8)

b. Synthesize the LC impedance function (8)

$$Z(S) = \frac{(S^2 + 1)(S^2 + 3)}{S(S^2 + 2)} \text{ in II Cauar Form}$$

Q.8 a. List the various properties of transfer functions of electrical networks. (8)

b. Determine the values of a, b and c for the given function $|F(j\omega)|$ to be a maximally flat magnitude function. (8)

$$F(S) = \frac{S + a}{S^2 + bS + c}$$

Q.9 a. An ideal voltage source in series with an impedance is shown in the following Fig.7. Obtain its equivalent current source across AB (4)

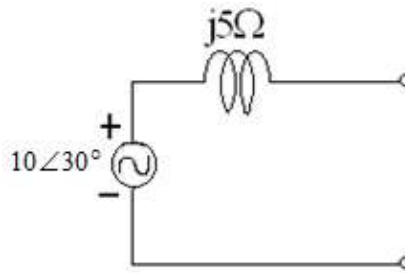


Fig.7

b. Calculate the following for half wave alternating current (8)

- Average value
- RMS value
- Form factor.

c. Describe the sine function using two oppositely rotating phasors. (4)