

Q.2 a. Explain with sketches P-well process of CMOS fabrication.

Answer: Page Number 14-15 of Text Book

b. What is the importance of Twin-Tub process? Sketch cross-sectional view of Twin-Tub Inverter.

Answer: Page Number 19 of Text Book

c. Mention the advantages of CMOS over Bipolar technology.

Answer: Page Number 22 of Text Book

Q.3 a. Starting from the fundamentals derive an expression for I_{ds} of n-MOS inverter in saturation region and linear region.

Answer: Page Number 29-32 of Text Book

b. What is Latch-up in CMOS? Sketch latch-up circuit for CMOS n-well process.

Answer: Page Number 59 of Text Book

c. For n-MOS enhancement transistor, $\mu_n = 215 \text{ cm}^2/\text{Vsec}$, Oxide capacitance (C_{ox}) = $2.3 \text{ fF}/\mu\text{m}^2$, drain current (I_d) = $100 \mu\text{A}$ and $W/L = 10$. Calculate Transconductance (g_m).

Answer:

W.K.T, $I_{ds} = \frac{\beta}{2} (V_{gs} - V_t)^2$ and $g_m = \beta(V_{gs} - V_t)$ from this we can write

$$\text{Transconductance } (g_m) = (2\beta I_{ds})^{1/2} = (2 \cdot C_{ox} \cdot \mu \cdot \frac{W}{L} \cdot I_d)^{1/2}$$

$$= (2 \times 2.3 \times 10^{-15} \times 215 \times 10 \times 100 \times 10^{-6}) = 314.4 \mu\text{mhos}$$

$g_m = 314.4 \mu\text{mhos}$

Q.4 a. Discuss λ -based design rules for wires and contacts.

Answer: Page Number 74 of Text Book

b. Draw stick-diagrams for n-MOS inverter, P-well CMOS inverter

(i) 3-input n-MOS NOR gate

(ii) 2-input CMOS (P-well) NOR gate

Answer: Page Number 234-235 of Text Book

Q.5 a. Show that the total delay of cascaded N number of CMOS inverters is $3.5 \text{ eN}\tau$.

Answer: Page Number 99-101 of Text Book

b. Explain how Super buffers can be used to achieve symmetrical transitions, when inverters are used to drive more capacitive loads.

Answer: Page Number 101-102 of Text Book

- c. Find the time constant (τ_p) of p-FET for the following parameters:
 $(W/L)_p = 8$, $K_p = 62 \mu\text{A}/\text{V}^2$, $V_{tp} = -0.85 \text{ V}$, $V_{DD} = 3.3 \text{ V}$, the total capacitance is 150 fF.

Answer:

The channel resistance of p-FET is given by $R_p = \frac{1}{\beta_p (V_{DD} - |V_{tp}|)}$

$$= \frac{1}{K_p \frac{W}{L} (V_{DD} - |V_{tp}|)} = \frac{1}{62 \times 10^{-6} \times 8 (3.3 - 0.85)}$$

$R_p = 822.9 \Omega$

Now $\tau_p = R_p \cdot C_p = 822.9 \times 150 \times 10^{-15} = 123.43 \text{ ps}$

$\tau_p = 123.43 \text{ ps}$

- Q.6** a. Write the scaling factors for the following device parameters.
 (i) Gate capacitance
 (ii) Saturation current I_{dss}
 (iii) Power speed product (P_T)

Answer: Page Number 115-118 of Text Book

- b. With truth table and stick diagram explain Bus arbitration logic for n-line bus.

Answer: Page Number 153-156 of Text Book

- Q.7** a. Explain the operation of 4x4 barrel shifter with schematic. What is the limitation of 4x4 crossbar switch?

Answer: Page Number 188 of Text Book

- b. Design a single bit adder and implement 4-bit ALU functions using adder elements.

Answer: Page Number 205-206 of Text Book

- Q.8** a. Explain with circuit diagram n-MOS and CMOS Pseudo-static memory cells.

Answer: Page Number 242 of Text Book

- b. Discuss briefly the ground rules for successful design.

Answer: Page Number 282-283 of Text Book

- Q.9** Write short notes on:

- (i) Design style and philosophy
 (ii) System partitioning
 (iii) Boundary Scan Test (BST)
 (iv) Built-In-Self-Test (BIST)

Answer:

- (i) Page Number 291 of Text Book
- (ii) Page Number 306 of Text Book
- (iii) Page Number 323 of Text Book
- (iv) Page Number 325 of Text Book

TEXT BOOK

Basic VLSI Design By D A Pucknell, Eshraghian Third Edition, PHI private Ltd.