

- Q.2 a. In the circuit of Fig. 1, $V_A = 2V$, $I_A = 2A$, $R_1 = 4\Omega$ and $R_2 = 3\Omega$. Find the Thevenin equivalent voltage V_{th} and impedance Z_{th} for the network to the left of terminals 1, 2.

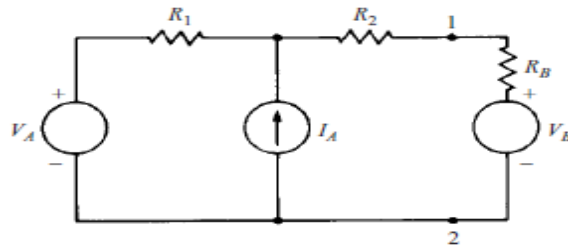


Fig.1

Answer:

Q:2

• With terminals 1-2 open circuited, no current flows through R_2 , by using KVL

(2x3)
$$\underline{V_{th}} = V_{12} = V_A + I_A R_1 = 2 + (2 \times 4) = \underline{10V}$$

• Z_{th} - With V_A replaced by a short and I_A replaced by an open circuit.

$$\underline{Z_{th}} = R_{Th} = R_1 + R_2 = 4 + 3 = \underline{7\Omega}$$

- b. Explain Duality. Obtain dual network for the circuit shown in fig.2.

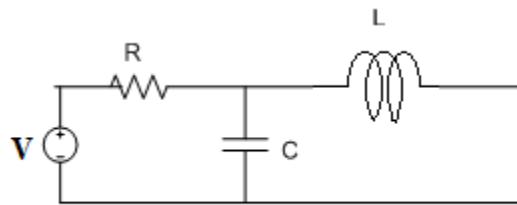


Fig.2

Answer:


Duality :- Networks which have identical describing differential equations are known as dual of each other, and the concept is known as DUALITY.

eg. dual of elements

$R \leftrightarrow G$ voltage source \leftrightarrow current source,
 $L \leftrightarrow C$

Q.3 a. Draw and explain switching characteristics of a diode.

Answer:

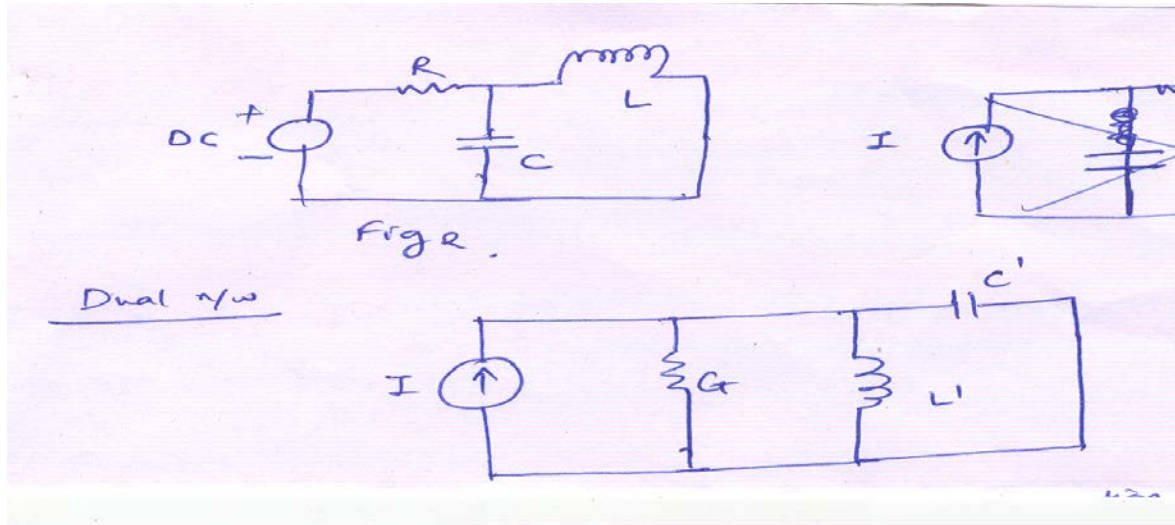

b. Plot the output voltage V_0

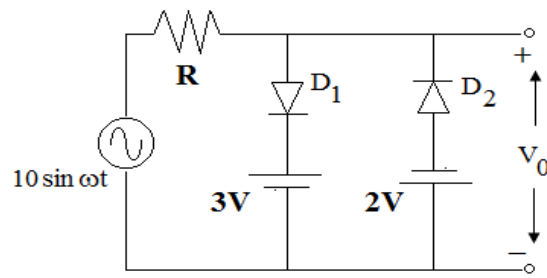


Fig.3

Answer: Topic 1.14 of Text Book 1

- c. Write short note on:
- (i) Transition and Diffusion capacitance
 - (ii) Zener diode as voltage regulator

Answer: Topic 1.13 of Text Book 1

Q.4 a. Explain the construction and operation of a n-channel E-MOSFET with suitable diagram and characteristics.

Answer: Topic 2.3 of Text Book 1

- b. The transistor of Fig.4 is provided with the fixed and self biased emitter resistance with $R_c = 4\text{ k}\Omega$, $R_E = 2\text{ k}\Omega$, $V_{cc} = 32\text{ V}$ and $I_C = 4\text{ mA}$.
- (i) Calculate the value of R_B if $\beta = 100$
 - (ii) What will be the percentage change in I_C if actual $\beta=40$?

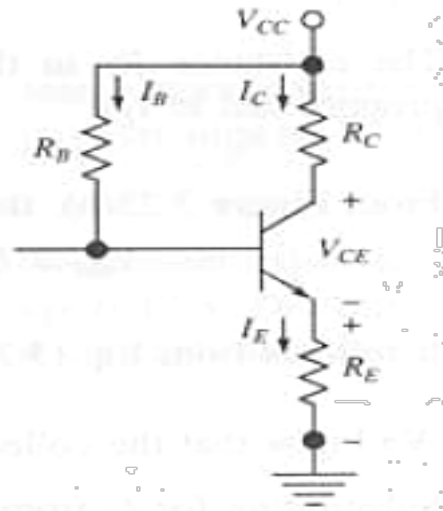



Fig. 4

Answer:

Condition.	Emitter junction	Collector junction	Region of operation	application
i) I FR	FB	RB	Active.	→ Amplification
ii) II FF	FB	FF	Saturation	→ Closed switch.
iii) III RR	RB	RB	Cut-off	→ open switch.
iv) IV RF	RB	FB	Inverted	→ Not used. (∵ Very poor transistor action).

c. Draw V-I characteristics of an SCR.

Answer:

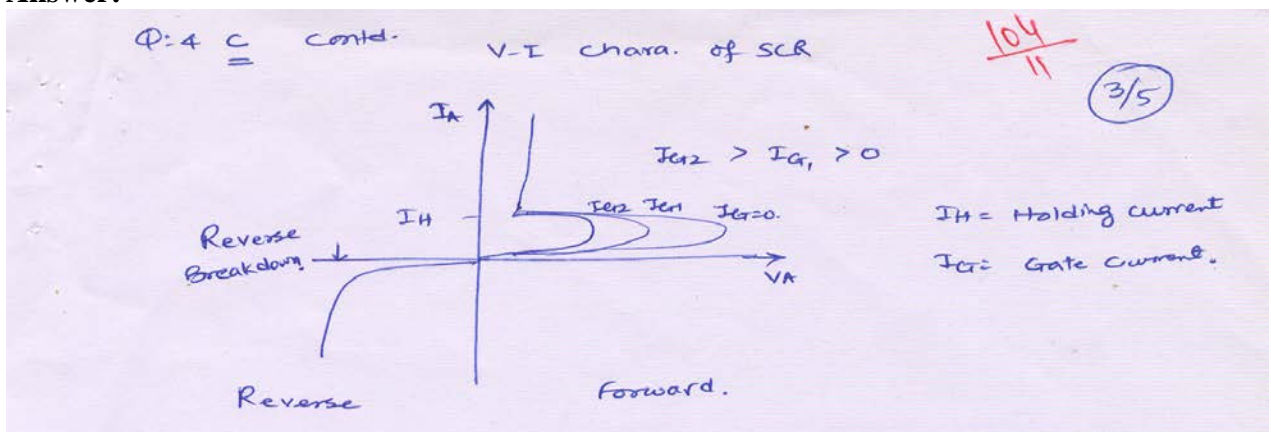

Q.5 a. Draw the small-signal model of Emitter follower and obtain the expression of voltage gain, current gain, input impedance and output impedance.

Answer:

Q.5
 (a) Given. $R_C = 4k\Omega$ $R_E = 2k\Omega$ $V_{CC} = 32V$ and $I_C = 4mA$.
 (i) Value of R_B if $\beta = 100$. (ii) Actual $\beta = 40$; $\Delta I_C = ?$

$$I_B = \frac{I_C}{\beta} = \frac{4}{100} = 0.04mA$$

$$V_{CC} = I_B R_B + V_{BE} + (I_B + I_C) R_E$$

$$32 = 0.04 \times R_B + 0.7 + (0.04 + 4) \times 2$$

$$\therefore R_B = 550k\Omega$$

$$32 = 550 I_B + 0.7 + (I_B + 4) \times 2$$

$$\therefore I_B = 0.04mA$$

$$I_C = I_B \times \beta = 40 \times 0.04 = 1.6mA$$

$$\Delta I_C = 4 - 1.6 = 2.4mA$$

$$= 60\% \text{ Reduction.}$$

b. Explain working of a Darlington pair amplifier in detail.

Answer: Topic 3.9 of Text Book 1

c. Write short note on CMOS.

Answer: Topic 3.2 of Text Book 1

Q.6 a. Explain working of tuned amplifier. Also state its merit and application.

Answer: Topic 4.4 of Text Book 1

b. A certain BJT transistor has $r_\pi = 2k\Omega$ and $\beta = 50$ at 1MHz and $\beta = 2.5$ at 20MHz. Determine f_T , f_β and C_π .

Answer:

(b) Given $r_\pi = 2k\Omega$ $\beta = 50$ at 1MHz.
 $\beta = 2.5$ at 20MHz.

$$f_T = \beta f_\beta = \beta_f \cdot f$$

$$f_T = 2.5 \times 20 = \underline{50MHz}$$

$$f_\beta = \frac{f_T}{\beta} = \frac{50}{50} = \underline{1MHz}$$

$$f_\beta = \frac{1}{2\pi C_\pi r_\pi}$$

$$1 \times 10^6 = \frac{1}{2\pi C_\pi 2 \times 10^3}$$

$$C_\pi = \frac{1}{2\pi \times 2 \times 10^3 \times 1 \times 10^6}$$

$$\underline{C_\pi \approx 50pF}$$

c. Write short note on cascaded amplifiers.

Answer: Topic 4.6 of Text Book 1

Q.7 a. Compare Class A, Class B, Class AB and Class C power amplifiers.

Answer: Topic 5.5 of Text Book 1

b. State performance parameters of power amplifier.

Answer:

- i) Collector efficiency = ac power output / dc power input.
 ii) Distortion -
 iii) Power dissipation capability -

c. A transistor supplies 2W for a 5 kΩ load. The zero-signal dc collector current is 35 mA and rises to 40 mA when signal is applied. Determine the percent second-harmonic distortion.

Answer:

$$I_c = 35 \text{ mA}$$

$$I_c + B_o = 40 \text{ mA}$$

$$\therefore B_o = 40 - 35 = 5 \text{ mA}$$

$$P_1 = B_1^2 \frac{R_L}{2}$$

$$\therefore B_1 = 28.3 \text{ mA}$$

$$B_2 = B_o = 5 \text{ mA}$$
 Second harmonic distortion.

$$D_2 = \left| \frac{B_2}{B_1} \right| \times \frac{5}{28.3} \times 100$$

$$= 17.66\% \text{ Ans.}$$

Q.8 a. Define feedback. Which type of feedback is used for oscillator circuit? Discuss feedback's effect on input and output impedance.

Answer:

Q.8 (a)
Feedback :- The process by which a fraction of output energy of device (amplifier) is injected back to its input is called feedback.
 (01 mark)

Type :- Positive feedback :- Used for oscillator circuit.
 (01 mark) Negative feedback :- used for amplifier.

Rest part :- Topic 6.4. Ret(F).

- b. A voltage series feedback amplifier has the following data: $A = -500$, $R_i = 1.5 \text{ k}\Omega$, $R_o = 50 \text{ k}\Omega$ and $\beta = (1/10)$. Calculate amplifier gain, input and output resistances. Also draw topology for the same

Answer:

(2x3) ~~Q.9~~ (a) Given $A = -500$, $R_i = 1.5 \text{ k}\Omega$, $R_o = 50 \text{ k}\Omega$ and $\beta = 1/20$. (2x4)

$1 + A\beta = 1 + 500 \times \frac{1}{20} = 26$

$A_f = \frac{-A}{1 + A\beta} = -\frac{500}{26}$

$A_f = 19.23$ amplifier gain.

$R_{if} = R_i (1 + A\beta) = 1.5 \times 26 = 39 \text{ k}\Omega$
(input resi.)

$R_{of} = \frac{R_o}{1 + A\beta} = \frac{50}{26} = 1.92 \text{ k}\Omega$
(output resi.)

Topology for voltage series feedback.

- Q.9** a. Write short notes:
 (i) Integrated resistors
 (ii) Integrated capacitors

Answer: Topic 9.9 & 9.10 of Text Book 1

- b. State characteristics of IC components.

Answer: Topic 9.12 of Text Book 1

- c. State levels of integration of IC fabrication.

Answer: Topic 9.14 of Text Book 1

TEXT BOOK

Electronic Devices and Circuits, I. J. Nagrath, PHI (2007)