

**Q.2** a. Enlist the various advantages of IC over discrete component circuits.

**Answer: 1.2 of Text Book I**

b. Draw basic differential amplifier and discuss transfer characteristics of an ideal operational amplifier.

**Answer: 2.4.1 & 2.4.2 of Text Book I**

c. Design an amplifier with a gain of +5 using one OP-AMP

**Answer: Page Number 49 of Text Book I**

**Q.3** a. State non-ideal DC characteristics of an op-amp. Explain any two of them in detail.

**Answer: 3.2 of Text Book I**

b. (i) Define Slew Rate of an op-amp

(ii) What causes the Slew Rate

(iii) How Slew Rate is measured

(iv) Can IC 741C be used for high frequency application?

**Answer: 3.3.4 of Text Book I**

**Q.4** a. Draw the characteristics of an ideal comparator and that of a commercially available comparator. Also list different types of comparators.

**Answer: Page Number 207 of Text Book**

**Q.5** a. Describe the operation of an Astable multivibrator using 555 timer.

**Answer: 5.4 of Text Book I**

b. Calculate the values of LSB, MSB and full scale output for an 8-bit DAC for the 0 to 10V range.

**Answer:**

(b) 8-bit DAC for 0 to 10V.  $(2^8 - 1 = 255)$   
 LSB =  $\frac{1}{255} \times 10V = 39.216V$   
 MSB =  $(\frac{1}{2})$  Full Scale = 5V.  
 Full Scale O/P = (Fullscale Voltage - 1LSB) =  $10V - 0.039216V = 9.960784V$

c. What is a voltage regulator? State only name of the circuits that are used to make a regulated power supply.

**Answer:**

**Q:5 (c)** A voltage regulator is an electronic circuit that provides a stable dc voltage independent of the load current, temp. and ac line voltage variations.  $(3/3)$   
 Four parts :- Reference voltage circuit, Error amplifier, series pass transistor, feedback n/w.  $(2M)$

- Q.6 a. Differentiate between positive logic and negative logic.  
 b. Perform the following conversions:  
 (i)  $(110011011001)_2 = (\text{---})_{10}$     (ii)  $(268)_{10} = (\text{---})_{16}$   
 (iii)  $(39.12)_{10} = (\text{---})_2$     (iv)  $(1054)_8 = (\text{---})_{10}$   
 (v)  $(2040.125)_{10} = (\text{---})_{16}$     (vi)  $(1001101.1011)_2 = (\text{---})_8$

Answer:

Q:6 (a)

Positive logic	Negative logic
1) logic state 1 $\equiv$ higher voltage level	Lower Voltage Level
2) logic state 0 $\equiv$ Lower voltage level	Higher voltage level.

}  $2 \times 2 = 4$

(b) (i)  $(110011011001)_2 = (\text{---})_{10}$  6x2

$\begin{matrix} 1 & 1 & 0 & 0 & 1 & 1 & 0 & 1 & 1 & 0 & 0 & 1 \\ / & / & / & / & / & / & / & / & / & / & / & / \\ 2048 & 1024 & 512 & 256 & 128 & 64 & 32 & 16 & 8 & 4 & 2 & 1 \end{matrix} = (3289)_{10}$

(ii)  $(268)_{10} = (\text{---})_{16}$

16	268	
16	16	Reminder 12: C
16	1	0: 0
2	1	1: 1

↑ 10C

cii)  $(39.12)_{10} = ( \quad )_2$  107/9

4/2

2	39	Remainder	
2	19	1 (LSB)	$0.12 \times 2 = 0.24$ 0 <span style="float: right;">MSB</span>
2	9	1	$0.24 \times 2 = 0.48$ 0
2	4	0	$0.48 \times 2 = 0.96$ 0
2	2	1	$0.96 \times 2 = 1.92$ 1
2	1	0	$0.92 \times 2 = 1.84$ 1
	1	0	

↑  
↓

$(1001011.00011\dots)_2$

civ)  $(1054)_8 = ( \quad )_{10}$

$10^3 \ 5^2 \ 4^1 \ 8^0 = (556)_{10}$

cv)  $(2040.125)_{10} = (7FB.2)_{16}$

16	2040	Remainder	
16	127	8	$.125 \times 16 = 2$
16	7	15 (F)	
		7	

v)  $(1001101.1011)_2 = ( \quad )_8$

$001 \ 001 \ 101 \ . \ 101 \ 100$   
↓    ↓    ↓    ↓    ↓  
1    1    5    5    4    =  $(115.54)_8$



Q.7 a. Why NAND and NOR gates are called universal gates?

Answer: 3.12 of Text Book II

b. Prove that the given identity  $Y = \overline{A+B}$  represents a NOR logic.


c. (i) Draw the logic circuit for the given identity  $Y = ABC + \overline{ABC} + B$

(ii) Simplify the expression and draw a logic circuit for the same.


Answer:

(b)  $Y = \overline{A+B}$  - NOR Gate. or  $\overline{Y} = A+B$

A	B	Y	$\overline{Y}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0




(2x2 = 4M)



$Y = \overline{A+B}$

(c)  $Y = ABC + \overline{ABC} + B$

(i) Logic circuit (2M)

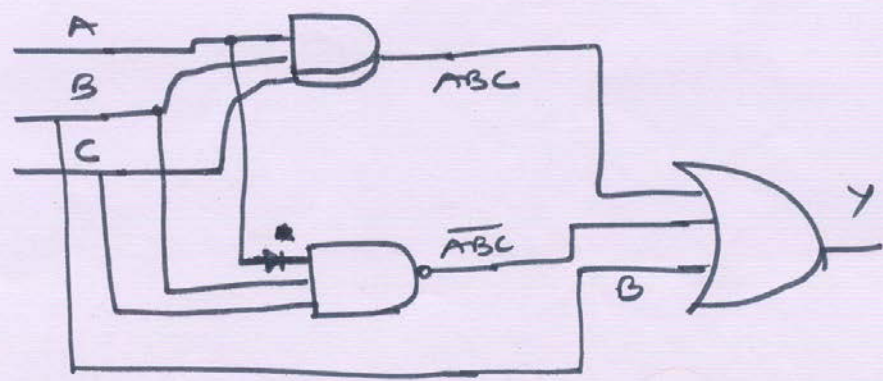

(ii) simplification.

$$Y = ABC + \overline{ABC} + B$$

$$= 1 + B$$

$$= 1$$

**Q.8** a. What is Priority encoder? Draw & explain the truth table of decimal to BCD priority encoder.

**Answer: Page Number 593 of Text Book**

b. Design a Full Adder Circuit consisting of three inputs A, B,  $C_{IN}$  and two outputs S,  $C_{OUT}$ .

**Answer: Page Number 320 of Text Book**

**Q.9** a. Write short notes on:-

(i) NAND gate latch

(ii) Clocked D FF

**Answer: 9.8 & 5.4 of Text Book**

### Text Books

1. Linear Integrated Circuits, Revised Second Edition, D Roy Choudhury, Shail B. Jain, New Age International Publishers.

2. Digital Systems – Principles and Applications, Ninth Edition, Ronald J Tocci, Neal S Widmer and Gregory L. Moss, Pearson Education, 2008.