

Q.2 a. How integrated resistors are fabricated? Explain diffused resistor method in detail?

Answer:


ANS 2(a) The basic technique for obtaining a resistor in integrated circuit is by utilising the bulk resistance of a defined volume of semiconductor region.

Diffused Resistor: In this method, resistor is formed in one of the isolated regions of epitaxial layer during base or emitter diffusion common to bipolar transistor fabrication.

This type of resistor is very economical. The value of the resistance depends upon the surface geometry. That is, length, width and upon the diffused impurity profile. In this context, a very useful quantity sheet resistance is defined as diffused layers are very thin. The resistance of the sheet of material can be written as

$R_s = \frac{PL}{Lt} = \frac{P}{L}$  if consider the square  $L \times L$  of a material of resistivity  $\rho$ , thickness  $t$ , and cross sectional area  $A = L \times t$  shown in fig. The resistance of these sheet of material resistors can be expressed in terms of the sheet resistance  $R_s$  and surface dimensions  $L$  and  $w$

 $R = \rho \frac{L}{wt}$  where ratio  $L/w$  is called the aspect ratio of the surface geometry and is, therefore, the effective number of square contained in the resistor.



therefore the effective number of square contained in the resistor. The base resistor in the range of  $20 \Omega$  to  $300 \text{ k}\Omega$  can be easily fabricated.

due to medium resistivity p type base region

b. Why aluminium is usually used for metallization of most ICs?

Answer:

- (b)
- (i) It is relatively a good conductor
  - (ii) It is easy to deposit aluminium films using vacuum deposition
  - (iii) Aluminium make good mechanical bonds with silicon
  - (iv) Aluminium forms low resistance, non-rectifying contact with p type silicon and the heavily doped n type silicon

c. Explain the self aligning property of a polysilicon gate MOSFET

Answer:


- (c)
- The polysilicon-gate provides self alignment of the gate with the source and drain. In the conventional metal gate structure, the gate electrode is normally designed to overlap the edges of the source and drain region by about  $5\mu\text{m}$  to avoid any masking errors. This, however, results in small overlap capacitance  $C_{gs}$  between gate G and source S and  $C_{gd}$  between gate G and drain D. These capacitances are of order of 1 to 3 pF and lower the speed of operation and increases the power consumption. The silicon gate due to self aligning property eliminates these capacitances.

Q.3

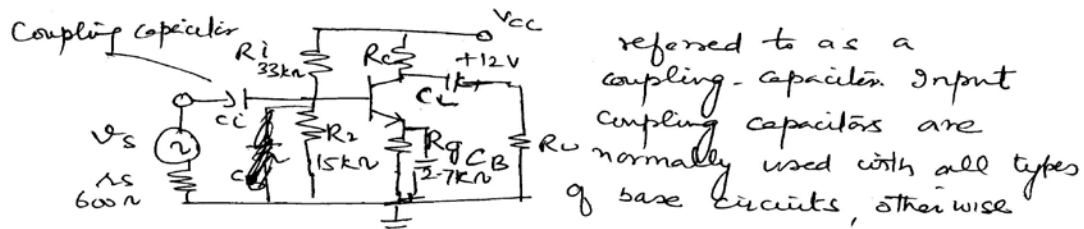a. Explain the need for coupling and bypass capacitors in transistor circuits, and draw AC Equivalent circuit of CE amplifier.

Answer:

Ans: 3 The capacitor  $C_i$  is used to couple the signal source to the circuit input. Because  $C_i$  is an open circuit to direct currents,  $V_s$  does not affect the level of  $V_B$ . Capacitor  $C_i$  behave as a short circuit for the ac signals, so that the signal voltage ( $V_s$ ) appears at the transistor base as shown in fig. In this case the signal is said to be ac coupled to the circuit input and  $C_i$  is




the circuit bias conditions will be altered. Due to coupling capacitor the supply voltage at the transistor collector terminal is reduced from  $V_{CC}$  to  $V = \frac{V_{CC} \times R_L}{R_C + R_L}$

and the collector resistance becomes

$$R_C = R_C \parallel R_L$$

This has the effect of altering the circuit dc load line and Q point. The capacitor  $C_o$  offers a short circuit to ac signals so that there is no feedback from the transistor collector to the base. When  $C_o$  is replaced with a short-circuit,  $R_B$  and  $R_{B2}$  appear in parallel with the circuit input and output respectively. Second problem of ac degeneration is eliminated by the emitter bypass capacitor  $C_e$ .

AC Equivalent circuit: Capacitors behave as short circuits to ac signals so in the ac equivalent circuit for a transistor circuit all capacitors must be replaced with short circuits because the dc supply voltage is not affected by the ac signals. Also all power supplies have large value capacitors at the output terminals, and these will offer short circuits to ac signals. Substituting short circuits in place of all the power supply and all capacitors in the circuit below fig gives ac equivalent circuit

 

Power supply and capacitors behave as ac short-circuits

if  $R_L$  is present, it appears in parallel with  $R_C$  in the ac equivalent circuit

- b. Use the simplified h-parameter model to derive equations for the current gain  $A_i$ , the input impedance  $R_{in}$ , the gain  $A_v$  and the output impedance  $R_{out}$  for the emitter follower circuit shown in Fig.2. Calculate the value of these parameters, assuming  $h_{ie} = 1100\Omega$ ,  $R_e = 10\text{ K}\Omega$ ,  $h_{fe} = 50$  and  $R_s = 1\text{ k}\Omega$


 


Fig.2

Answer:

3b Equivalent circuit of diagram 'b

 

$$A_v = \frac{V_o}{V_i} \approx \frac{h_{fe} i_b R_e}{h_{ie} i_b + R_e h_{fe} i_b}$$

$$= \frac{h_{fe} R_e}{h_{ie} + h_{fe} R_e} = 1 - \frac{h_{ie}}{R'_{in}}$$

$$R_{in} = \frac{V_i}{i_b} \approx \frac{h_{ie} i_b + h_{fe} i_b R_e}{i_b} = h_{ie} + h_{fe} R_e \approx h_{fe} R_e$$

$$R_{out} = \frac{V_o(oc)}{i_o(sc)} = \frac{i_b (R_s + h_{ie})}{h_{fe} i_b} = \frac{R_s + h_{ie}}{h_{fe}} =$$

$$A_i \approx 50 \quad R_{in} = 1.1\text{ k}\Omega + 50 \times 10\text{ k}\Omega \approx 500\text{ k}\Omega$$


$$A_v = 1 - \frac{1100}{50 \times 10^3} = 0.98 \quad R_{out} = \frac{1\text{ k}\Omega + 1.1\text{ k}\Omega}{50} = 42\Omega$$

$$R'_{out} = R_{out} \parallel R_e = 10\text{ k}\Omega \parallel 42\Omega = 42\Omega$$

 
- Q.4 a. Draw and explain the transfer characteristics of JFET. List the advantages of JFET.

Answer:

4a The transfer characteristics for an n channel JFET are a plot of  $I_D$  versus  $V_{GS}$ . The gate source voltage of a FET controls the level of the drain current, so the transfer characteristics is shown in fig.



(1)

 

The transfer characteristic extends from  $I_D = I_{DSS}$  at  $V_{GS} = 0$  to  $I_D = 0$  at  $V_{GS} = V_p$ . Fig. 2 shows that the drain-source voltage is

maintained constant.  $V_{GS}$  is adjusted in convenient steps and corresponding level of  $V_{GS}$  and  $I_D$  are recorded. The characteristic shows that as  $-V_{GS}$  is increased  $I_D$  is progressively reduced from  $I_{DSS}$  at  $V_{GS} = 0$  to  $I_D = 0$  at  $V_{GS} = -V_p$ . The transfer characteristic for a FET can be derived from the drain characteristics. A line is drawn vertically on the drain characteristics to represent a constant  $V_{DS}$  level.

- b. The constant current circuit shown in Fig.3 uses a JFET whose operation is described by the equation

$$I_D = I_{DSS}(1 - V_{GS}/V_P)^2, I_{DSS} = 8 \text{ mA} \quad \text{and} \quad V_P = 4 \text{ V}$$

- Draw the equivalent circuit as an amplifier
- Calculate the required value of  $R$  to give a current of 0.5 mA
- If the FET drain-source resistance  $r_{ds}$  is equal to 50 k $\Omega$  at  $I_D = 0.5$  mA, determine the incremental resistance of the circuit for the value of  $R$  calculated in (ii)


 


Fig.3

Answer:

 

(i) from the equation for  $I_D$

$$0.5 \times 10^{-3} = 8 \times 10^{-3} \left(1 + \frac{V_{GS}}{4}\right)^2 \therefore V_{GS} = -3V$$

But  $R = \frac{-V_{GS}}{I_D} = \frac{3V}{0.5 \text{ mA}} = 6 \text{ k}\Omega$

(iii) The output resistance is found from  $R_o = \frac{V_o(oc)}{i_o(sc)}$   
 with output open circuit  $V_o(oc) = -g_m V_i r_{ds}$   
 with output short circuit

$$V_{GS} = V_i + R i_o(sc) \quad \text{But} \quad i_o(sc) = \frac{-g_m V_{GS} r_{ds}}{R + r_{ds}}$$

$$i_o(sc) = \frac{-g_m r_{ds}}{R + r_{ds}} (V_i + R i_o(sc))$$

$$i_o(sc) = \frac{g_m r_{ds} V_i}{R + (1 + g_m R) r_{ds}} = \frac{V_o(oc)}{i_o(sc)} = R + (1 + g_m R) r_{ds}$$


$$= 356 \text{ k}\Omega$$

Q.5 a. Draw and explain the circuit of complementary emitter follower.

Answer:

Two BJTs connected to function as emitter follower. One is npn and other is pnp, the devices are selected to have similar parameters, so they are complementary transistors. The circuit is termed as a complementary emitter follower. ~~As shown in fig~~  
 Complementary emitter follower have similar signal applied simultaneously to both device bases as shown in fig. Transistor  $Q_1$  conducts during the positive half cycle of the signal and it pulls the output voltage up to follow the input. During this time  $Q_2$  base-emitter

 
function is reverse biased. For the duration of the negative half cycle of the input  $\phi_1$ , base-emitter junction is reversed and  $Q_2$  conducts, pulling the output down to follow the input. Thus, the complementary emitter follower is a large scale circuit with the low output impedance. Another advantage is, this circuit does not require transformer. This saves on weight and cost.



- b. Draw the circuits of opto-coupler with SCR and Triac and briefly explain these circuits.

Answer:

 (a) Darlington output type : the output stage provides much higher CTR than a BJT photo transistor output stage but it also has slower response time




(a) Darlington output

(b) & (c) SCR & triac type are a light activated SCR and light activated triac type. They are used with the kind of control circuits where high electrical isolation between the triggering circuit and the control device is an additional requirement. CTR does not apply to SCR and Triac output stages instead, the LED current needed to trigger the thyristor is of interest.




(b) SCR output

 

(c) Triac output

- c. Show that maximum collector efficiency of class A transformer coupled power amplifier is 50%.

Answer:

 

ckt (i) shows the transformer coupled class A amplifier. Under zero signal conditions, the effective resistance in the collector ckt is that of the primary winding of the transformer. The primary resistance has a very small

value and is assumed zero. Therefore dc load line is a vertical line rising from  $V_{CC}$ . When signal is applied the collector current will vary about the operating point Q. In order to get maximum ac power output, the peak value of collector current due to signal alone should be equal to the zero signal collector current  $I_C$ .

During the peak of the positive half cycle of the signal, the total current is  $2I_C$  and  $V_{CE} = 0$ . During the negative peak of the signal, the collector current is zero and  $V_{CE} = 2V_{CC}$ .

$\therefore$  Peak-to-peak collector-emitter voltage is

$$V_{CE(p-p)} = 2V_{CC}$$

peak to peak collector current  $I_C(p-p) = 2I_C$

$$= \frac{V_{CE(p-p)}}{R'_L} = \frac{2V_{CC}}{R'_L}$$

where  $R'_L$  is the reflected value of load  $R_L$  and appears in the primary of the transformer. If  $n (= N_p/N_s)$  is the turn ratio of the transformer then  $R'_L = n^2 R_L$ .

dc power input  $P_{DC} = V_{CC} I_C = I_C^2 R'_L$

Max. ac output power  $P_{AC(max)} = \frac{V_{CE(p-p)} \times I_C(p-p)}{8}$

$$= \frac{2V_{CC} \times 2I_C}{8} = \frac{1}{2} V_{CC} I_C = \frac{1}{2} I_C^2 R'_L$$


$$\text{Max Collector Efficiency} = \frac{P_{AC(max)}}{P_{DC}} \times 100 = \frac{\left(\frac{1}{2}\right) I_C^2 R'_L}{I_C^2 R'_L} \times 100 = 50\%$$

Q.6 a. What is the need of negative feedback in OPAMP?

Answer:



 (a) An op-amp is almost always operated with negative feedback i.e. a part of the output is fed back in phase opposition to the input. With negative feedback, the voltage gain can be reduced and controlled so that op-amp can function as linear amplifier. In addition to providing a controlled and stable gain, negative feedback also provides for control of the input and output impedances and amplifier bandwidth.



b. Define the following parameter and give their values for IC 723

- |                         |                           |
|-------------------------|---------------------------|
| (i) Input bias current  | (ii) CMMR                 |
| (iii) Output resistance | (iv) Input offset voltage |

Answer:


(b) (a) The average of the currents entering into (-) input and (+) input terminals of an op-amp. Its value is 500 nA for 741C.

(b) CMMR is typically 90 dB.

(c) It is the resistance between the output terminal of the op-amp and the ground. It is 75  $\Omega$  for the 741C op-amp.

(d) It is the voltage that must be applied between the input terminals of an op-amp to nullify the output for 741C, the maximum value is 6 mV.

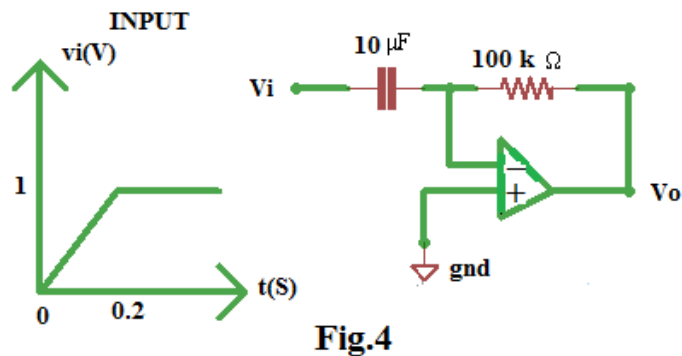- c. For the differentiator circuit shown in Fig.4, find:
- the expression for the output voltage
  - the output voltage for the given input.



Answer:

*current is  $\frac{V}{R}$*   
 (i) for the differentiator, the output voltage is given by


$$V_o = -R_f \frac{dV_i}{dt} = -(100k\Omega \times 10\mu F) \frac{dV_i}{dt}$$

$$= -(100 \times 10^3 \Omega) \times (10 \times 10^{-6} F) \frac{dV_i}{dt} = - \frac{dV_i}{dt}$$

 (ii) Since the input voltage is straight line between 0 & 0.2sec the output voltage is

$$V_o = \frac{dV_i}{dt} = \frac{(1-0)}{0.2} = -5V$$


Therefore between 0 to 0.2s the output voltage is constant at -5V for  $t > 0.2s$  the input is constant so that output voltage is zero.



 
- Q.7** a. Draw and explain Sample and Hold circuit using OPAMP. Draw input and output waveform of the circuit.

Answer:

Ans 7(a) A sample and hold circuit samples an input signal and holds onto its last sampled value until the input is sampled again. The circuit shown in fig



The n channel E-MOSFET works as a switch and is controlled by the control voltage  $V_c$  and the capacitor  $C$  stores the charge. The analog signal  $V_i$  to be sampled is applied to the drain of E-MOSFET and the control voltage  $V_c$  is applied to its gate. When  $V_c$  is positive the E-MOSFET turns on and the capacitor  $C$  charges to the instantaneous value of input  $V_i$  with a time constant  $[R_o + r_{DS(on)}]C$ . Here  $R_o$  is the output resistance of the voltage follower  $A_1$  and  $r_{DS(on)}$  is the resistance of the MOSFET when on. Thus the input voltage  $V_i$  appears across the capacitor  $C$  and then at the output through the voltage follower  $A_2$ . When  $V_c$  is zero the E-MOSFET is off. The capacitor  $C$  is now facing the high input impedance of the voltage follower  $A_2$  and hence cannot discharge. The capacitor holds the voltage across it. The time period  $T_H$  of  $V_c$  during which the voltage across the capacitor is held constant is called hold period.

 

Input and output waveforms

- b. For the circuit shown in the Fig.5 assuming that the input current is negligible, show that  $v_o/v_i = f(R_2, R_1, A)$  and that it may be approximately to  $v_o/v_i = -(R_2/R_1)$ .  
Explain the purpose of  $R_3$

 


Fig.5

Answer:

7(b) Let the non-inverting input be  $v_g$ . current in  $R_1$  be  $i_1$ , and the current in  $R_2$  be  $i_2$

$$\therefore i_1 = \frac{v_i - v_g}{R_1} \quad \text{and} \quad i_2 = \frac{v_g - v_o}{R_2}$$

But since amplifier input current is zero  $i_1 = i_2$

$$\therefore \frac{v_i - v_g}{R_1} = \frac{v_g - v_o}{R_2}$$

Now  $v_o = -A v_g$ , where  $A$  is the openloop gain

$$\therefore \frac{v_i + \frac{v_o}{A}}{R_1} = - \frac{\left( \frac{v_o}{A} + v_o \right)}{R_2}$$

$$\therefore \frac{v_o}{v_i} = - \frac{R_2}{R_1} \left( \frac{1}{1 + \frac{R_1 + R_2}{A R_1}} \right) \quad \text{for large values of } A \quad \frac{v_o}{v_i} \approx - \frac{R_2}{R_1}$$

The purpose of  $R_3$  is to reduce the effect of input offset voltage due to input bias current


$$\therefore R_3 = \frac{R_1 R_2}{R_1 + R_2}$$

- Q.8 a. What are the applications of comparators? Explain the operation of zero crossing detector.

Answer:

8(a) Various important applications of comparator are  
 (i) Zero crossing detector (ii) Window detector  
 (iii) Time marker generator (iv) Pulse meter  
 (v) Level detector (vi) Square wave generator

 Zero crossing detector: When one of the input of comparator is connected to ground. It is known as zero crossing detector because output changes when input crosses 0V. The circuit and waveform shown in fig



When the input signal is positive going, the output is driven to positive maximum value. When the input crosses the zero axis and begins to go negative, the output is driven to negative maximum value.


Q.9 Write Short notes on any **TWO** of the following:

- (i) 723 general purpose voltage regulator
- (ii) Flash type A/D convertor
- (iii) IC voltage regulator

Answer:

9(a) Current Boosting. The maximum current that 723 IC regulator can provide is 140mA. which is not sufficient for many applications and it is possible to boost the current level simply by adding a boost Transistor  $Q_1$  to the voltage regulator. The collector current of the pass transistor  $Q_1$  comes from the unregulated dc supply. The output current from  $V_o$  terminal drives the base of the

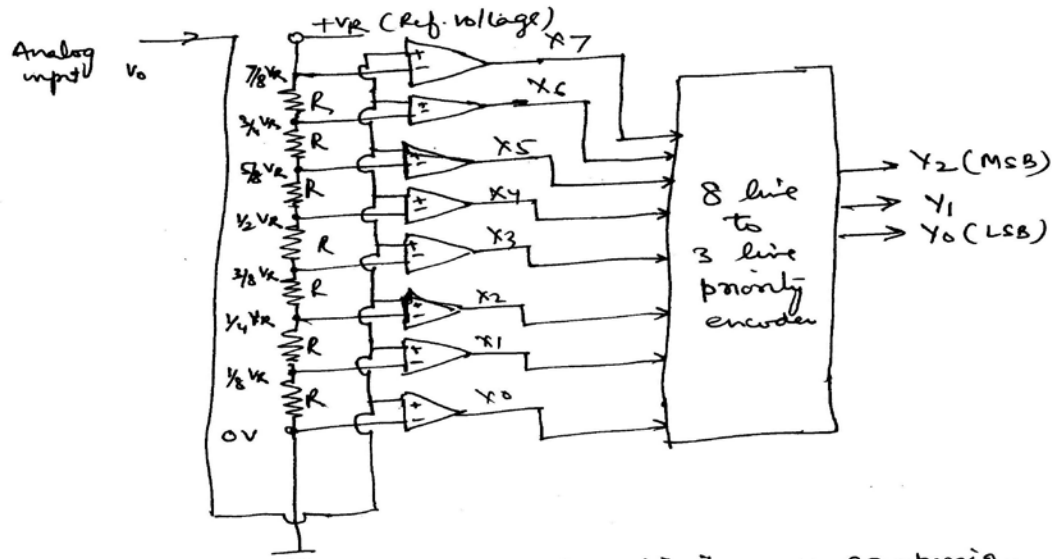- 9 (b) It is the fastest and most expensive type ADC. 3 bit A/D converter shown in fig consist of a resistive divider network, 8 op-amp comparators and 8 bit to 3 encoder.



At each node of the resistive divider, a comparison voltage is available. Since all the resistors are of equal

value, the voltage levels available at the nodes are equally divided between the ref. voltage  $V_R$  and ground.

The purpose of the circuit is to compare the analog input voltage  $V_a$  with each of the node voltages. The circuit has the advantage of high speed as the conversions take place simultaneously rather than sequentially and disadvantage that the number of comparators required almost doubles for each added bit. For large value of  $n$ , the more complex is the priority encoder.

### Text Books

1. Electronic Devices and Circuits, Fourth Edition, David A Bell, PHI (2006).
2. Linear Integrated Circuits, Revised Second Edition, D. Roy Choudhury, Shail B. Jain, New Age International Publishers.