

**Q.2a. Explain the photolithography process used in IC fabrication.**

Ans : Page 7 to 8 of reference 2

**b. Explain various methods used for deposition of thin films.**


Ans : Page 31 to 32 of reference 2

**Q.3 a. Draw the Common Emitter circuit and draw its h-parameter equivalent circuit and derive the expressions for**

- (i) Input Resistance                      (ii) Output Resistance  
(iii) Voltage Gain                        (iv) Current Gain

Ans : Page 254 to 257 of reference 1

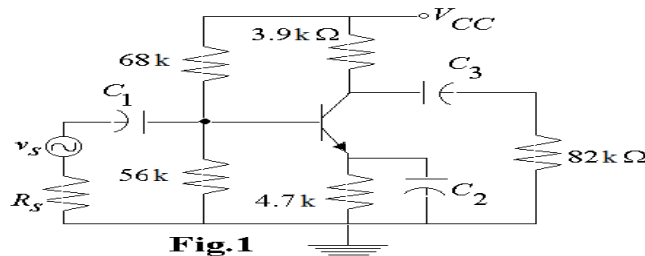**b. Calculate  $R_i$ ,  $R_o$ ,  $A_v$  for the circuit shown in Fig.1 below with  $h_{ie} = 2.0 \text{ k}\Omega$ ,  $h_{fe} = 75$  and  $h_{oe} = 1.0 \mu\text{s}$ .**



Ans : Page 258 to 259 of reference 1

**Q.4a. Explain the operating principle of N-channel JFET.**


Ans : Page 346 to 347 of reference 1

**b. Explain how an N-channel JFET can be used as an amplifier**

Ans : Page 364 to 365 of reference 1

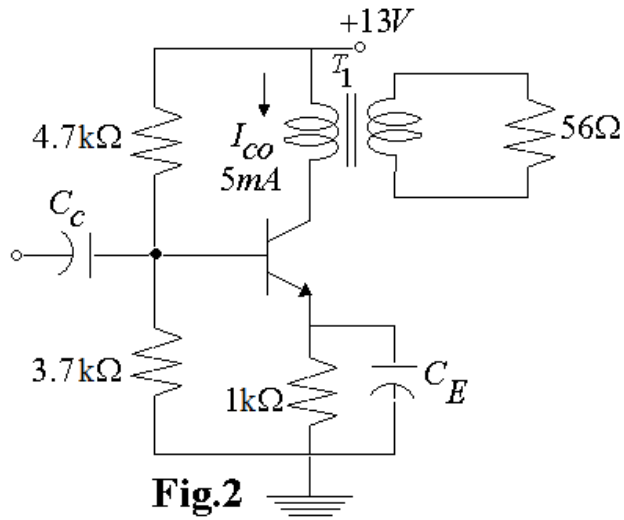**Q.5a. Calculate the maximum efficiency of Class A amplifier shown below in Fig.2.**

Assume that the transformer has an efficiency of 80%. (8)



Ans : Page 814 of reference 1

**b. Explain the operation of Class B power amplifier with a neat circuit diagram.**

Ans : Page 815 of reference 1

**Q.6a. Explain the basic differential amplifier.**

Ans : Page 53 to 55 of reference 2

**b. Define the term “Slew Rate” for an Op-Amp and derive the expression for maximum input frequency at which undistorted output voltage is obtained.**

Ans : Page 123 to 125 of reference 2

**Q.7 a. Explain the V to I and I to V converter circuits using Op-Amp.**

Ans : Page 146 to 147 of reference 2

**b. Draw the circuit of integrator using Op-Amp and derive the expression for its output.**

Ans : Page 168 to 169 of reference 2

**Q.8 a. Explain, with a neat circuit diagram, the working of Schmitt Trigger using an OP-Amp.**

Ans : Page 212 to 214 of reference 2

**b. Draw the circuit of monostable multivibrator using 555 IC and derive the expression for time period T.**

Ans : Page 312 to 314 of reference 2

**Q.9 a. Explain the working of a Regulated Power Supply with a neat diagram.**

Ans : Page 240 to 241 of reference 2

**b. Explain, with a neat diagram, the working of Successive Approximation Type Analog to Digital Converter.**

Ans : Page 240 to 241 of reference 2

#### Text Book

**1. Electronic Devices and Circuits, Fifth Edition, David A Bell, OXFORD UNIVERSITY PRESS, Thirteenth impression 2010.**

**2. Linear Integrated Circuits, 4th Reprint 2011 Edition, D. Roy Choudhury, Shail B. Jain, New Age International Publishers**