

**Q.2 a. Perform the following conversions:**

(i)  $(3742)_8 = (?)_{10}$

(ii)  $(2A64)_{16} = (?)_2$

(iii)  $(2047)_{10} = (?)_{16}$

(iv)  $(1101011)_2 = (?)_{10}$

**Answer: Pages 26 to 40 (Chapter 1) of Text Book**

**b. With the help of neat sketch explain serial and parallel transmission.**

**Answer : Pages 16 to 17 (Chapter 1) of Text Book**

**c. Draw functional diagram of digital computer.**

**Answer: Pages 18 to 20 (Chapter 1) of Text Book**

**Q.3 a. Draw the symbol of AND and NOR gate and explain their working using truth table**

**Answer: Pages 62 to 64 (Chapter 3) of Text Book**

**b. Simplify the following expression using K map and implement it using logic gate.**


$$Y = \overline{ABC} + \overline{A}BC + ABC + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C$$

**Answer:**

Give equation is


$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}BC + ABC + A\bar{B}\bar{C} + A\bar{B}C$$

The K-MAP is

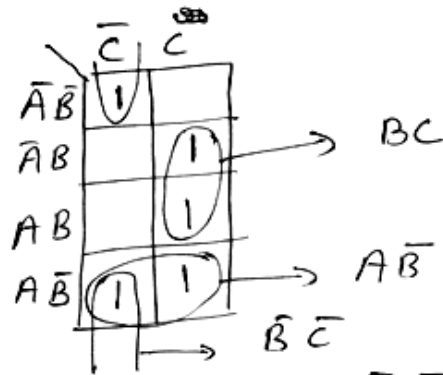

$$\therefore Y = BC + A\bar{B} + \bar{B}\bar{C}$$

Logic diagram of given equation is

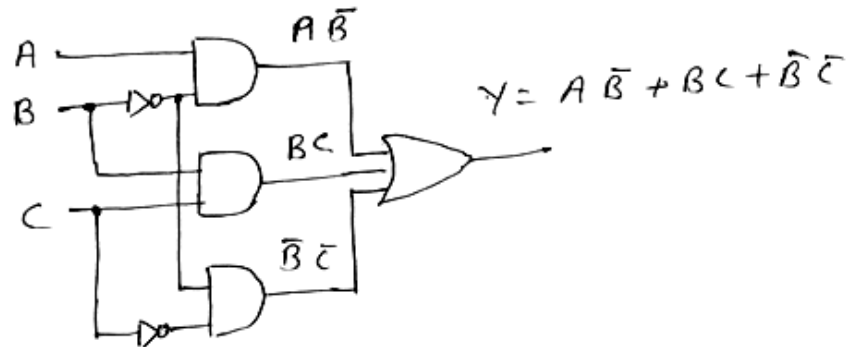

c. Draw the symbols and truth tables of XOR gate and XNOR gates.

Answer: Pages 134 to 135 (Chapter 4) of Text Book

Q.4 a. Draw logic circuit of 4-bit BCD adder and explain its working.

Answer : Pages 297 to 301 (Chapter 6) of Text Book

b. Perform the following operation:

(i)  $(45)_{10} - (23)_{10}$  Using 2's complement method.

(ii)  $(10111)_2 - (100)_2$

(iii)  $(385)_{10} + (118)_{10}$  Using BCD addition.

(iv) Represent decimal value -12 as an 8-bit signed binary value.

Answer:

(i)  $45 - 23$  using 2's complement.

$$(45)_{10} = 101101$$

$$(23)_{10} = 010111$$

$$1^{\text{st}} \text{ complement of } 23 = 101000$$

$$2^{\text{nd}} \text{ complement of } 23 = 101000 + 1 = 101001$$

$$\text{So } (45)_{10} - (23)_{10} = \begin{array}{r} 101101 \\ 101001 \\ \hline \end{array}$$

$$\text{Discard } \leftarrow \textcircled{1}010110$$

Since there is carry generated, so result is positive number, and magnitude is given by.

$$(010110)_2 = 16 + 4 + 2 = (22)_{10}$$

(ii) Binary subtraction

$$\begin{array}{r} 10111 \\ - 100 \\ \hline 10011 \end{array}$$

$$\text{Answer} = 10011$$

(ii)  $(385) + (118)_{10}$  Using BCD

$$\begin{array}{r}
 385 = 0011\ 1000\ 0101 \\
 118 = 0001\ 0001\ 1000 \\
 \hline
 503 \quad 0100\ 1001\ 1101 \rightarrow \\
 \quad \quad \quad \quad \quad \quad \quad 0110 \\
 \quad \quad \quad \quad \quad \quad \quad \quad \quad 1 \\
 \hline
 \quad \quad \quad 0100\ 1010\ 0011 \\
 \quad \quad \quad \quad \quad \quad 1\ 0110 \\
 \hline
 \text{Ans} \rightarrow 0101\ 0000\ 0011
 \end{array}$$

Last term.  
 Invalid, so  
 Add 0110  
  
 Middle term  
 Invalid so  
 Add 0110

**Q.5 a.** Draw the circuit of 4 bit serial in parallel out shift register and explain its working.

**Answer:** Pages 385 to 386 (Chapter 7) of Text Book

**b.** Draw logic circuit of 4 bit ring counter and explain its working with the help of truth table, waveforms and state diagram.

**Answer:** Pages 370 to 375 (Chapter 7) of Text Book

**Q.6 a.** What is encoder? Explain working of octal to binary encoder.

**Answer:** Pages 517 to 518 (Chapter 9) of Text Book

**b.** What is de-multiplexer? Draw logic diagram of 1:8 de-multiplexer and explain its working.

**Answer:** Pages 536 to 538 (Chapter 9) of Text Book

**Q.7 a.** Draw the logic diagram NOR gate latch and its working using truth table.

**Answer:** Pages 188 to 189 (Chapter 5) of Text Book

- b. What is frequency division? How can flip flop be used for this application? Also list other applications of flip flop.

Answer: Pages 224 to 226 (Chapter 5) of Text Book

- Q.8 a. Explain working principle of decade counter with suitable logic diagram.

Answer: Pages 328 to 330 (Chapter 7) of Text Book

- b. What are synchronous counters? Design a Mod-6 synchronous counter using J-K Flip-Flops.

Answer: Pages 340, 341 and 362 to 367 (Chapter 7) of text Book

- Q.9 a. What is RAM? Distinguish between SRAM and DRAM.

Answer: Pages 694 to 704 of Text Book

- b. How many address bits are required to access a 32 K memory?

Answer: Pages 694 to 704 (Chapter 11) of Text Book

The memory stores  $32\text{ K} = 32 \times 1024 = 32768$  words  
Thus there are 32768 memory locations.. Since  
 $32768 = 2^{15}$ , it requires a 15 bit address  
code to specify one of 32768 addresses.

- c. What is ROM? Draw  $16 \times 8$  ROM architecture and explain its working.

Answer: Pages 673 to 675 (Chapter 11) of Text Book

### TEXT BOOK

- i. Digital Systems – Principles and Applications, Ronald J Tocci, Neal S. Wildmer, Gregory L. Moss, Tenth Edition, Pearson Education, Copyright 2009.