Find the value of v(t) using Laplace transform if **O.2a.**  $V(s) = \frac{s+2}{s(s+1) + (s+3)}$ What is its value at  $t = 0^+$  and  $t = \infty$ ? Grivey that Q 2(a)  $V(s) = \frac{s+2}{s(s+1)(s+3)} = \frac{a_1}{s} + \frac{a_2}{s+1} + \frac{a_3}{s+3}$  $a_{1} = \frac{5+2}{(5+1)(5+3)} = \frac{2}{3}$  $Q_{2} = \frac{s+2}{s(s+3)} = \frac{-1+2}{-1(-1+3)} = -\frac{1}{2}$  $q_3 = \frac{5+2}{5(5+1)} = \frac{-3+2}{-3(-3+1)} = -\frac{1}{6}$ Therefore, V(S) = 2/3 - 1/2 - 6 Taking inverse Laplace S+1 S+3  $\frac{1}{29(t)} = \int = \int \frac{2/3}{5} - \frac{1}{5} - \frac{$  $\mathcal{D}(t) = \frac{2}{3}u(t) - \frac{1}{2}e^{-t} - \frac{1}{6}e^{-3t}$ At t=0,  $V(0^+)=0$  and at  $t=\infty$   $V(\infty)=\frac{2}{3}$ Making use of initial Value theorem  $\frac{U(t)}{t \Rightarrow 0} = sV(s) = \lim_{s \Rightarrow \infty} \frac{S(s+2)}{S(s+1)(s+3)} = 0$ 

1

and making use of final value theorem  

$$2s(t) = sV(s) = \frac{s(s+2)}{s(s+2)(s+3)} = \frac{2}{3}$$

**b.State and prove the shifting theorem of Laplace Transform.** 

(32(b) Shifting Theorem  
This theorem states that Laplace of any function  
shifted or deget delayed by a time interval of  
a is 
$$e^{-as}$$
 to times the transform of the function  
Proof: - Let any function  $f(t)$  is shifted by  
time a. The shifted function may be  
represented by  $f(t-a)$ .  $u(t-a)$   
Choosing a new variable x, by definition,  
we have  
 $F(s) = \int f(x) e^{-sx} dx$ .  
Let  $x = t-a$ , the above expression will become  
 $F(s) = \int f(t-a) \bar{e}^{-s(t-a)} d(t-a)$   
 $= \int_{0}^{\infty} f(t-a) e^{-s(t-a)} dt$   
 $= e^{as} \int_{0}^{\infty} f(t-a) e^{-as} dt$ 

The lower limit of integration may be changed  
from a to o if 
$$f(t-a)$$
 is multiplied by  $u(t-a)$   
Therefore,  $F(s) = e^{as} \int f(t-a) u(t-a)e^{-st} dt$   
 $= e^{as} d [f(t-a) u(t-a)] dt$ .  
 $or = L[f(t-a) \cdot u(t-a)] = e^{-as} f(s)$   
Thus the shifting theorem is proved.

## Q.3 a. State and explain Thevenin's theorem. What are its limitations?

Therewin's Theorem Therewin's Theorem state that "Any two terminal Consisting of time linear impedances and generators may be replaced by an e.m.f. acking in series with an impedance. The e.m.f. is the open circuit voltage at the terminals and the impedance is the impe-dance viewed at the terminals when all the gene-rators in the network down beau put local but rators in the network have been replaced by impedances equal to their internal impedances." Network of Generators & Linear Empedances B ZI B Thevenin Source.



$$I_{2} = \frac{E \frac{Z_{3}}{Z_{1}+Z_{3}}}{Z_{1}Z_{2}+Z_{2}Z_{3}+Z_{3}Z_{1}} + Z_{L}} Or I_{2} = \frac{V_{0}C}{Z_{AB}+Z_{L}}$$
where  $Z_{AB} = \frac{Z_{1}Z_{2}+Z_{2}Z_{3}+Z_{3}Z_{1}}{Z_{1}+Z_{3}}$  &  $Voc = \frac{E^{2}}{Z_{1}+Z_{3}}$   
Now open circuit Voc which appear across AB  
of Figur (a).  
 $Voc = \frac{E^{2}Z_{3}}{Z_{1}+Z_{3}}$   
and if E short circuited, then impedance ZAB  
Viewed at the lenwinal AB will be.  
 $Z_{AB} = \frac{Z_{2}Z_{1}+Z_{2}Z_{3}+Z_{3}Z_{1}}{Z_{1}+Z_{3}}$   
Hence proved.  
Limitation of Therewin Theorem  
(1) Therewins theorem cannot be applied to a valuer  
which contains non linear impedances.  
(2) Therewin's theorem cannot be applied for the  
power Consumed integnally, although it gives  
power in the load cornelly.  
(3) This theorem cannot be used for determining  
the efficiency of the circuit.

b.Apply the superposition theorem to the network shown in Fig.1 and obtain the current in the (3 + j4) Ohm impedance.



Let V, acts above, then total impedance Z, of the circuit is given by  $Z_1 = 5 + \frac{(3+j4)!}{3+j4!} = 5!83+j2!5 = 6!35L23!3$ Current I, in the circuit =  $\frac{V_1}{Z_1} = \frac{50 \angle 90}{6.35/23.3} = 7.87 \angle 66.8^{\circ}$ Suppose I's's the current through (3+4j) when only Vi acts  $I' = I_{1} \frac{j5}{2+j9} = 7.87 \angle 66.8^{\circ}, \frac{j5}{3+j9} = 7.4.14 \angle 85.5$ Now let V2 acts alone, the total impedance of the  $Z_2 = j5 + \frac{5(3+4j)}{8+j4} = 2.5+j6.25 = 6.74/68.2^{\circ}$ Circuit Z2 Thus the current Iz in the circuit  $I_2 = \frac{V_2}{Z_2} = \frac{50L^0}{674L^{68} \cdot 2^\circ} = 7.42L^{-68} \cdot 2^\circ$ Suppose I" is the current through (3+j4) when only V2 acts I''= - (7.42 1-68.2°). 5 8+14 = 4.15 L85.3° The minus sign gives the I" the same direction as the branch current I shown in the diagram. The total current in the (3+j4) of branch is I = I' + I'' = 4114 285.3° + 4.15 285.3° = 8.30 285.3° Henre 8.30 L 85.3° Amp (Approximate) euvrent is Amp. Flowing in the (3+i4) r impedance. MANDERATION.



## Q.4 a. Find the z-parameters for the resistive network shown in Fig.2

$$\begin{split} I_{5} \times I = V_{1} - \dots \cdot \textcircled{0} \\ 2 I_{5} = 3 V_{1} - \dots \cdot \textcircled{0} \\ I_{6}(0.5+1) + 3 V_{1} = 0.5 I_{2} - \dots \cdot \textcircled{0} \\ 0.5(I_{2}-I_{6}) = V_{2} - \dots \cdot \textcircled{0} \\ From Eqs (i) A(i), we have \\ I_{5} = V_{1} = 0 \\ Hence from equation (i) A(i) A(i) = V_{2} - 0.72V_{2} = I_{2} - I_{6} - \dots \cdot \textcircled{0} \\ From eqs (i) I_{6}(1.5) + 0 = 0.5I_{2} \\ 0.7 I_{6} = \frac{0.5}{1.5} I_{2} = \frac{1}{3} I_{2} \\ Put Value of I_{6} in equation (10) \\ 2V_{2} = I_{2} - I_{6} = I_{2} - \frac{1}{3} I_{2} = \frac{2I_{2}}{3} \\ \dots V_{2} = \frac{1}{3} I_{2} \\ Therefore Z_{22} = \frac{V_{2}}{I_{2}} |_{I_{1}=0} = \frac{1}{3} \Lambda \\ & Z_{22} = \frac{V_{1}}{I_{2}} |_{I_{1}=0} = 0 \\ \hline Z_{11} = -I \Lambda , Z_{12} = 0 \\ Z_{21} = -I \Lambda , Z_{22} = \frac{1}{3} \Lambda \end{split}$$

b. The z-parameters of a two port network are  $Z_{11} = 10 \Omega$ ,  $Z_{22} = 20\Omega$ ,  $Z_{12} = Z_{21} = 20\Omega$ . Find the ABCD parameters of this two port network.

Q 4(b) Given 
$$|z_{11} = 10 \Omega$$
,  $z_{22} = 20 \Omega$ ,  $z_{12} = z_{21} = 5 \Omega s$ .  
We Know that ABCD parameters related to  
 $z$  parameter as follows  

$$A = \frac{Z_{11}}{Z_{12}} = \frac{10}{5} = 2 \Phi$$

$$B = \frac{Az}{Z_{21}} = \frac{Z_{11}Z_{22}-Z_{12}Z_{21}}{Z_{21}} = \frac{10 \times 20 - 5 \times 5}{5}$$

$$B = \frac{175}{5} = 35 \Omega$$

$$C = \frac{1}{Z_{21}}, = \frac{1}{-5} = 0.2 \text{ mho}$$

$$D = \frac{Z_{22}}{Z_{21}} = \frac{20}{5} = 4 M$$
[Note 2 marks for each parameter]

Q.5 a. The circuit shown in Fig.3 represents a parallel resonant circuit where  $R_L$  is the ohmic resistance of the inductor L. Find the resonant frequency of the circuit. (8)



(8)



b. A 220 V, 100 Hz AC source supplies a series LCR circuit with a capacitor and a coil. If the coil has 50 m $\Omega$  resistance and 5 mH inductance and resonant frequency of the circuit is 100 Hz, than find the value of capacitor. Also calculate Q factor and half power frequencies of the circuit.

Q.6 a. Define and explain phase velocity and group velocity of a uniform transmission line.

@ 6 (a) The velocity of propagation along the line based on the observation of charge in phase along the line. Since the charge of 271 in phase angle represents One cycle in time 't' and occurs in a distance of one wave length >, they X=2p\*t=2p×1 we know that  $\lambda = \frac{2\pi}{B}$  where  $\beta$  is phase shift.  $\frac{1}{B} = \frac{2\pi}{B} f = \frac{1}{B}$ Group Velocity :-In case of distortion less or loss less line Bphase shift is not a constant multiple of w. As a result of this the components in a complex waveform wormally Shipt in phase relation during propagation. This phe-nomenon is known as dispersion which results in distortion propagation is group velocity.

Thus group velocity is defined as the velocity of the envelope of a complex signal. It is denoted by the letter Up. MODERATION. In the transmission of modulated wave, pulses and transmission through wave guides. frequencies being transmitted and B, and B2 be the corresponding phase constant, then the group velocity 29 will be given as  $\mathcal{V}_g = \frac{\omega_2 - \omega_1}{\beta_2 - \beta_1} = \frac{d\omega}{d\beta}$ due is evaluated at the carrier of centre frequences Also we know that Up=  $\frac{w}{\beta}$  --- () differentiating w.r. t. 20, we get  $\frac{d\upsilon_p}{d\upsilon} = \frac{1\cdot\beta - \omega \frac{d\beta}{d\upsilon}}{\beta^2} = \frac{1 - \frac{\omega}{\beta} \left(\frac{d\beta}{d\omega}\right)}{\beta^2}$ B ол  $\beta \cdot \frac{dv_p}{dw} = 1 - v_p \cdot \frac{1}{v_q}$ on  $\frac{\partial p}{\partial g} = 1 - \beta \frac{d^2 p}{dw}$ on  $\partial g = \frac{\partial p}{1 - \beta \cdot \frac{d^2 p}{dw}}$ 

Put value of 
$$\beta$$
 from equation  $D$ , we get  
 $2g = \frac{29p}{1 - \frac{10}{20p}}$ 
MODERATION  
 $2g = 2p$ , when  $\frac{d2p}{dw} = 0$   
This is consistant with the definition of  
group velocity.  
 $X = - X = - X$ 

b.The primary constants of a line per loop km are  $R = 196 \Omega$ ;  $C = 0.09 \mu$ F; L = 7.1mH and leakage conductance is negligible. Calculate the characteristic impedance and the propagation constant at angular frequency of 5000 radians/sec.

Q.7 a. Derive expression for input impedance of open and short circuited line and show that characteristic impedance  $Z_0 = \sqrt{Z_{OC} \times Z_{SC}}$ 

b.A 100 km long transmission line is terminated by a resistance of 200 ohm. It has characteristics impedance  $Z_0 = 600 \angle 0^\circ$  ohms, attenuation constant  $\alpha = 0.01$  neper / km, phase shift constant  $\beta = 0.03$  rad / km. Find the reflection coefficient and the impedance.



$$= 600 \left[ \frac{1+0.675 (\cos 16.2 + 3\sin 16.2)}{1-0.675 (\cos 16.2 + 3\sin 16.2)} \right] = 600 \left[ \frac{1+0.675 (\cos 16.2 + 3\sin 16.2)}{1-0.675 (\cos 96 + 3o.2)} \right]$$
  
$$= 600 \left[ \frac{1+0.65 + 30.19}{1-0.65 - 30.19} \right] = 600 \left[ \frac{1.65 + 30.19}{0.35 - 30.19} \right]$$
  
$$= 600 \left[ \frac{1.65 + 30.19}{0.35 - 30.19} \right] \times \left[ \frac{0.35 + 30.19}{0.35 + 30.19} \right]$$
  
$$= 600 \left[ \frac{0.5414 + 30.382}{0.1586} \right] = 3760 (0.5414 + 30.382)$$
  
$$Z_{3M} = (2003 + 31416) \Omega$$

Q.8 a. Explain the operation and use of a quarter wave transformer.

Dipole Antenna (28(9) We know that the input impedance Zin of a uniform transmission line in terms Rin. Zo My of secondary line constants Zo Main Trasmission Line  $\overline{Z_{in}} = Z_0 \frac{Z_R \cosh Pl + Z_0 \sinh Pl}{Z_0 \cosh Pl + Z_R \sinh Pl}$ Since high prequency line can be considered loss pree, x=0 resulting Zo  $Z_{JN} = Z_{0} \frac{Z_{R} \cos h j \beta l + Z_{0} \sin h j \beta l}{Z_{0} \cos h j \beta l + Z_{R} \sin h j \beta l} = Z_{0} \frac{Z_{R} \cos \beta l + j Z_{0} \sin \beta l}{Z_{0} \cos \beta l + j Z_{R} \sin \beta l}$ P= jBonly, we have For the line which is quarter wave length 1=7/4 But  $\beta = \frac{2\pi}{\lambda}$ MODERATION.  $\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{4} = \frac{\pi}{2}$ Put value of B1 in above equation, we get

 $Z_{in} = Z_{0} \frac{Z_{R} \cos \frac{\pi}{2}}{Z_{0} \cos \frac{\pi}{2}} + j Z_{R} \sin \frac{\pi}{2} = Z_{0} \frac{Z_{0}}{Z_{R}} = \frac{Z_{0}^{2}}{Z_{R}}$ OR ZO= ZiuiZR This means that the product of the super impedance and load impedance is equal to the square of the characteristic impedance of line. The disadvantage of quarter wave transformer is Impedance Zo', by means of a X wave transformer is Impedance 20', by means of a X wave transformer is the transmission line having characteristic Impedance Zo', by means of a X wave transformer is Impedance Zo', by means of a X wave transformer is The disadvantage of quarter wave transformer is that it is sensitive to change in frequency.

- b. A low loss line with  $Z_0 = 70 \Omega$  terminates in an impedance of  $Z_R = 115 j80$ . The wave length of the transmission is 2.5 metres; using the smith chart find:
  - (i) Standing wave ratio
  - (ii) Maximum and minimum line impedance
  - (iii) Distance between load and first voltage maximum





Thus, maximum line impedance 70×2.7= 189 ohms minimum normalised line impedance = 0.36+jo maximum line impedance = 70×0.36=25.21 (iii) lmax = length of arc RP' measured on wave length = 0.198 X = 0.198 X 2.5 metre = 0.495 metre Scale





b.Design m-derived low pass filter having a design impedance of 600  $\Omega$  and cut-off frequency of 5000 Hz. The frequency of infinite attenuation is 6250 Hz.

Given that  

$$f_{e} = 5000 \text{ H}_{3}, \text{ Rk} = 600 \text{ A}, f_{00} = 6250 \text{ H}_{3}.$$

$$LPF \text{ for constant R}$$

$$L = \frac{R_{k}}{\pi \text{ fc}} = \frac{600}{3.14 \times 5000} = 38.2 \text{ mH}$$

$$C = \frac{1}{\pi \text{ Rk}te} = \frac{1}{3.14 \times 6000000} = 0.106 \text{ MF}$$
To obtained moderived LPF, the value of m JJ  

$$m = \sqrt{\left(1 - \left(\frac{t_{c}}{t_{00}}\right)^{2}\right)} = \sqrt{1 - \left(\frac{5000}{6250}\right)^{2} - \sqrt{1 - (0.8)^{2}}}$$
Or  $m = \sqrt{0.36} = 0.6$ 
The elements of moderived LPF, T section will be  

$$\frac{mL}{2} = \frac{0.6 \times 38.2}{2} \text{ mH} = 11.46 \text{ mH}$$

$$mC = 0.6 \times 0.106 \text{ MF} = 0.0636 \text{ MF}$$
and  $\frac{1-m^{2}}{4m} L = \frac{1-0.36}{40.06} \times 38.2 \text{ mH} = 10.1867 \text{ mH}$ 
The required moderived LPF will be.  

$$11.46 \text{ mH} = 11.46 \text{ mH}$$

$$The required moderived LPF will be.$$

$$11.46 \text{ mH} = 10.1867 \text{ mH}$$

## **TEXT BOOKS**

1. Network Analysis; G. K. Mittal; 14th Edition (2007) Khanna Publications; New Delhi

2. Transmission Lines and Networks; Umesh Sinha, 8th Edition (2003); Satya Prakashan, Incorporating Tech India Publications, New Delhi