

- Q.2** a. What is power electronics? Why is it needed? List out the applications of power electronics.

Answer: Refer Page Numbers 2,3,14 & 15

- b. What is the basic difference between a PN junction power diode and an ordinary PN junction diode? Discuss various principal ratings for power diodes.

Answer: Refer Page Numbers 19, 27 & 28.

- Q.3** a. Explain the operating principle of N-channel IGBT with a neat diagram. Draw the ideal IGBT V-I Characteristics.

Answer: Refer Page Numbers 62 & 63.

- b. Draw and explain the V-I characteristics of a Power BJT.

Answer: Refer Page Numbers 41 & 42

- Q.4** a. What is Silicon Controlled Switch? Draw and explain its structure, symbol and equivalent Circuit.

Answer: Refer Page Numbers 111 & 112.

- b. Explain two-transistor model of SCR with a neat circuit diagram.

Answer: Refer Page Numbers 75 & 76

- c. A gate-triggering circuit for an SCR provides a train of pulses with a frequency of 100 Hz and a pulse width of 2 ms. If the pulse has a peak power of 2 W. Find the average power dissipated by the gate.

Answer: Pulse Period $T = \frac{1}{f} = \frac{1}{100} = 10ms$

$$\text{Duty Cycle } (d) = \frac{T_{ON}}{T} = \frac{2}{10} = 0.2$$

Therefore, the **Average Power Dissipated by the gate** is

$$P_{O(avg.)} = 0.2 \times 2 = 0.4W$$

- Q.5** a. With neat diagram, explain the working of Single Phase Full Wave Semi-Controlled Bridge Rectifier with an inductive load. Draw its various waveforms.

Answer: Refer Page Numbers from 175 to 178.

- b. A Single Phase Full-wave controlled rectifier with an inductive load is connected to a 120 V source. The resistive portion of the load is equal to 10 Ω . If the delay angle (α) is 30°. Find
- (i) average load voltage
 - (ii) average load current
 - (iii) form factor
 - (iv) rectifier efficiency

Answer: Given data : Source Voltage (V_s) = 120 V
Load Resistance (R) = 10 Ω
Delay Angle (α) = 30°

The peak load voltage (V_m) is given by:

$$V_m = \sqrt{2}XV_s = \sqrt{2}.X(120) = 208V$$

- (i) Average Load Voltage,

$$V_{o(avg.)} = \frac{2}{\pi}V_m \cos \alpha = \frac{2}{\pi}(208)(\cos 30^\circ) = 115V.$$

- (ii) Average Load Current, $I_{o(avg.)} = \frac{115}{10} = 11.5Amp.$

- (iii) Form Factor, $FF = \frac{V_{o(RMS)}}{V_{o(avg.)}} = \frac{120}{115} = 1.04.$

- (iv) Rectifier Efficiency, $\eta = \frac{V_{o(avg.)}}{V_{o(RMS)}} = \frac{115}{120} = 0.96 = 96\%.$

- Q.6** a. Draw the circuit of Three Phase Full Wave Half-Controlled Bridge Rectifier with freewheeling diode (FWD). Explain its working with the help of voltage & current waveforms, when delay angle is less than 60°.

Answer: Refer Page Numbers from 254 to 258.

- b. A three-phase half-wave controlled rectifier connected to a three-phase, 280 V, 60 Hz AC source supplies power to a 10Ω resistive load. If the delay angle is 20° . Find
- maximum output current
 - average output voltage
 - average output current
 - SCR average current

Answer: **Given Data:** The maximum output voltage (V_L) is equal to the V_m .
Hence (V_L) = (V_m) = 208 V and $R = 10 \Omega$.

$$\text{The Phase Voltage, } V_{phase} = \frac{V_L}{\sqrt{3}} = \frac{208}{1.732} = 120 \text{Volts.}$$

The peak load voltage (V_m) is given by:

$$V_m = \sqrt{2} X V_{phase} = \sqrt{2} X 120 = 170 \text{Volts.}$$

- Maximum Output Current, $I_m = \frac{V_m}{R} = \frac{170}{10} = 17 \text{Amp.}$
- Average Output Voltage,
 $V_{o(avg.)} = 0.827 V_m \cos \alpha = (0.827)(170)(\cos 20^\circ) = 132 \text{Volts.}$
- Average Output Current, $I_{o(avg.)} = \frac{V_{o(avg.)}}{R} = \frac{132}{10} = 13.2 \text{Amp.}$
- SCR Average Current, $I_{SCR(avg.)} = \frac{I_{o(avg.)}}{3} = \frac{13.2}{3} = 4.4 \text{Amp.}$

- Q.7** a. What is Buck-Boost DC Chopper? Draw its circuit diagram and explain its operation for the ON state and OFF state.

Answer: **Refer Page Numbers from 295 to 298**

- b. What is DC chopper? Explain its principle of operation with circuit diagram and various waveforms.

Answer: **Refer Page Numbers from 269 to 272.**

- Q.8** a. Draw the circuit of basic or Half-Bridge Inverter. Explain its working. List out the industrial applications of inverters.

Answer: **Refer Page Numbers from 305 to 307**

- b. What is the necessity of pulse width modulated inverter? Draw the circuit diagram of single phase full-wave pulse-width modulated bridge inverter. Explain its working with output waveforms.

Answer: Refer Page Numbers 321 & from 324 to 326.

- Q.9** a. Discuss the principle of the integral cycle control method. Give its applications.

Answer: Refer Page Numbers 357 & 358.

- b. What is meant by static switch? Compare the advantages and disadvantages of semiconductor switches over mechanical switches.

Answer: Refer Page Numbers 411 & 412.

TEXT BOOK

- I. Power Electronics for Technology, First Impression (2006), Ashfaq Ahmed, Purdue University - Calumet, Pearson Education.