

**Q2 (a) Classify ICs on the basis of applications, devices used and chip complexity.**

**Answer** Article 1.2 -1.3 of Text Book I

**Q2 (b) In the differential amplifier circuit shown below, the transistors have identical characteristics and their  $\beta = 100$ . Determine the**


**(i) Output voltage**

**(ii) The base currents and**

**(iii) The base voltages taking into account the effect of the  $R_B$  and  $V_{BE}$ .**

**Assume  $V_{BE} = 0.7$  Volts,  $R_B = 25K\Omega$ ,  $R_C = 12K\Omega$  and  $R_E = 8K\Omega$ .**

**$V_{EE} = -12V$ ,  $V_{CC} = +12V$**

 

**Answer**

**Ans:**

$$\text{Tail current, } I_T = \frac{V_{EE}}{R_E} = \frac{12V}{8k} = 1.5mA$$

The collector current in transistor Q2 is half thus tail current (i.e. 0.75mA) because each transistor gets half the tail current.

$$\therefore V_{out} = V_{cc} - I_c \cdot R_C = 12 - (0.75)(10k)$$

$$V_{out} = 4.5V$$

$$\text{Tail current } I_T = \frac{V_{EE} - V_{BE}}{R_E} = \frac{12 - 0.7}{8k}$$

$$I_T = 1.41mA$$

$$V_{out} = V_{cc} - \frac{I_T}{2} \times R_C = 12 - \frac{1.41m}{2} \times 12k$$

$$V_{out} = 3.54$$

$$\text{And Tail current, } I_T = \frac{V_{EE} - V_{BE}}{R_E + \frac{R_B}{2\beta dc}}$$

$$I_T = \frac{12 - 0.7}{8k + \frac{25k}{2 \times 100}}$$

$$I_T = 1.390 \text{ mA}$$

And output voltage,

$$\begin{aligned} V_{out} &= V_{cc} - \frac{1}{2} I_T \cdot R_c \\ &= 12 - \frac{1}{2} \left( \frac{1.390}{2} \text{ m} \right) (12k) \end{aligned}$$

$$V_{out} = 3.66 \text{ v}$$

If the results obtained are compared, we find that the results obtained improve with each refinement, but the improvement is not significant.

$\therefore$  The ideal tail current is 1.41 mA

$$\therefore I_B = \frac{I_c}{\beta} = \frac{0.75 \text{ m}}{100} = 7.5 \mu\text{A}$$


$$\therefore V_B = -I_B \cdot R_B = -(7.5 \mu)(25k)$$

$$V_B = -0.1875 \text{ v}$$

**Q3 (a) Explain what you understand by ‘offset voltage’ and ‘offset current’ of op-amp. Discuss with a neat circuit diagram the technique used for minimizing offset voltage and offset current in an inverting amplifier.**

**Answer** Article 3.2 – 3.4 of Text Book I

**Q3 (b) Calculate the output voltage ‘V<sub>o</sub>’ for the following non-inverting op-amp summer with V<sub>1</sub> = 2V and V<sub>2</sub> = -1V**

 

**Fig.2**

**Answer**

**Ans:**

$$V_o = \left( \frac{[R_2 V_1 + R_1 V_2]}{[R_1 + R_2]} \right) \cdot \left( \frac{[R + R_f]}{R} \right)$$

If in the summer circuit the value of resistance are selected as  $R_1 = R_2 = R$  and

$$R_f = 2R. \text{ Then}$$

$$V_o = - \left[ \frac{(2R) V_1}{R} + \frac{(2R) V_2}{R} \right]$$

$$= - [2(V_1 + V_2)]$$

$$= - [2(2 - 1)] = -2 \text{ V}$$

**Q4 (a) Explain Schmitt trigger with the help of transfer characteristics. Also obtain the expression of hysteresis voltage  $V_H$  and output waveform for sinusoidal input signal.**

Answer Article 5.3 of Text Book I

**Q4 (b) The input to an op-amp differentiator circuit is a sinusoidal voltage of peak value  $10\mu\text{V}$  and frequency of 2 kHz. If the values of differentiating components are given as  $R = 40\text{ k}\Omega$  and  $C = 3\mu\text{F}$ , determine the output voltage of differentiator circuit.**

Answer

**Ans:**

$$V_{in} = V_{\max} \sin 2\pi ft = 10 \times 10^{-6} \sin 2\pi \cdot 2000 \cdot t$$

$$V_{in} = 10 \sin 4000\pi t \mu\text{v}$$

$$\text{Scale factor} = CR = 3 \times 10^{-6} \times 40 \times 10^3 = 0.12$$

$$\therefore V_{out} = -CR \frac{dV_c}{dt} = -0.12 \frac{d}{dt} (10 \sin 4000\pi t) \mu\text{v}$$

$$V_{out} = -0.12 \times 10 \times \frac{d}{dt} (\sin 4000\pi t) \mu\text{v}$$

$$V_{out} = 1.2 (4000\pi \cdot \cos 4000\pi t) \mu\text{v}$$

$$V_{out} = 15.0816 (\cos 4000\pi t) \mu\text{v}$$

**Q5 (a) Explain the working of R-2R Ladder Digital to Analog Converter.**

Answer Article 10.2 of Text Book I

**Q5 (b) Explain Monostable multivibrator circuit operation using 555 timers. Also, determine the frequency of output signal.**

Answer Article 8.3 of Text Book I

**Q5 (c) Explain the working of Series Op-Amp Regulator**

Answer Article 6.2 of Text Book I

**Q6 (a) Differentiate between analog and digital signals.**

Answer Article 1.1 of Text Book II

**Q6 (b) Explain the concept of Parity bits with reference to error detection.**

Answer Article 2.10 of Text Book II

**Q6(c) Convert the following:**

(i)  $(5A34F)_{16}$  to binary

(ii)  $(56)_{10}$  to Gray Code

(iii)  $(93)_{10}$  to Excess-3 Code

**Answer**

(i)  $(0\ 1\ 0\ 1\ 1\ 0\ 1\ 0\ 0\ 0\ 1\ 1\ 0\ 1\ 0\ 0\ 1\ 1\ 1\ 1)_2$

(ii)  $56 = (111000)_2 = (100100)$

(iii) Ex-3 representation of 93 is 11000110

**Q7( a) Simplify the Boolean function ‘F’ together with don’t care conditions ‘d’ in sum of Products**

$$F(w, x, y, z) = \sum(0,1,2,3,7,8,10)$$

$$d(w, x, y, z) = \sum(5,6,11,15)$$

**Answer**

Sum of products

	$y'z'$	$y'z$	$yz$	$yz'$
$w'x'$	1	1	1	1
$w'x$		X	1	X
$wx$			X	
$wx'$	1		X	1

$$F = w'z + x'z'$$

**Q7 (b) State and prove De Morgan’s theorem using truth table.**

Answer Article 3.11 of Text Book II

**Q7 (c) Show that NAND gate is a Universal gate.**

Answer Article 3.12 of Text Book II

**Q8 (a) Explain the 4-bit parallel binary adder.**

Answer Article 6.10 of Text Book II

**Q8 (b) Write a short note on 8: 1 Multiplexers**

Answer Article 9.5 of Text Book II

**Q9 (a) Draw and explain the working of NAND-gate latch.**

Answer Article 6.1 of Text Book II

**Q9 (b) Distinguish between synchronous and asynchronous counters. Design a 3-bit UP-DOWN synchronous counter.**

**Answer**

Difference between synchronous and asynchronous counter:

1. In synchronous counters synchronized at the same time. But in the case of asynchronous counter the output of first flip-flop is given as the clock input of the next flip-flop.
2. In synchronous counter the output occurs after nth clock pulse if number of bits are N. But in asynchronous counter the output is derived by previous one that's why n+1 step or clock pulse will be required.

**Design of 3 bit UP DOWN counter:-**

For  $M = 0$ , it acts as an UP counter and for  $M = 1$  as a DOWN counter. The number of flip-flop required is 3. The input of the flip-flops are determined in a manner similar to the following table.

**Truth Tables**

Direction M	Present State			Required FlipFlop					
	$Q_3$	$Q_1$	$Q_0$	$J_0$	$K_0$	$J_1$	$K_1$	$J_2$	$K_2$
0	0	0	0	1	X	0	X	0	X
0	0	0	1	X	1	1	X	0	X
0	0	1	0	1	X	X	0	0	X
0	0	1	1	X	1	X	1	1	X
0	1	0	0	1	X	0	X	X	0
0	1	0	1	X	1	1	X	X	0
0	1	1	0	1	X	X	0	X	0
0	1	1	1	X	1	X	1	X	1
1	0	0	0	1	X	0	X	1	X
1	1	1	1	X	1	1	X	X	0
1	1	1	0	1	X	X	0	X	0
1	1	0	1	X	1	X	1	X	0
1	1	0	0	1	X	0	X	X	1
1	0	1	1	X	1	1	X	0	X
1	0	1	0	1	X	X	0	0	X
1	0	0	1	X	1	X	1	0	X

From truth table

The  $J_0 = K_0 = 1$

$$J_1 = K_1 = Q_0\overline{M} + \overline{Q_0}M$$

$$J_2 = K_2 = \overline{M}Q_1Q_0 + M\overline{Q_1}\overline{Q_0}$$

Connecting the equations of all the flip-flops into NAND realization circuit

$$J_1 = K_1 = Q_0\overline{M} + \overline{Q_0}M$$


$$= \overline{Q_0\overline{M} + \overline{Q_0}M}$$

$$= \overline{Q_0\overline{M}} \cdot \overline{\overline{Q_0}M}$$

$$J_2 = K_2 = \overline{M}Q_1Q_0 + M\overline{Q_1}\overline{Q_0}$$

$$= \overline{\overline{M}Q_1Q_0 + M\overline{Q_1}\overline{Q_0}}$$
 
$$= \overline{\overline{M}Q_1Q_0} \cdot \overline{M\overline{Q_1}\overline{Q_0}}$$



Logic diagram of 3 bit UP – DOWN Counter

Text Book

1. Linear Integrated Circuits, Revised Second Edition, D Roy Choudhury, Shail B. Jain, New Age International Publishers.
2. Digital Systems – Principles and Applications, Ninth Edition, Ronald J Tocci, Neal S Widmer and Gregory L. Moss, Pearson Education, 2008.