 


Q2 (a) Explain basic n MOS transistors.

Answer

Basic NMOS transistors:- are formed in p-type substrate of moderate doping. The source and drain regions are formed by diffusion of n-type impurities through suitable masks into these areas to give the desired n-impurity concentration and give rise to depletion region which extend mainly in the more lightly doped p-region. Thus source and drain are isolated from one another by two diodes. Connections to the source and drain are made by a deposited metal layer.



The channel may also be established so that it is present under the condition $V_{gs} = 0$ by implementing suitable impurities in the region between source and drain during manufacture and prior to deposit the insulating and gate. next

Q2 (b) Explain the thermal aspects of processing nMOS and CMOS devices.

Answer: Page Number 17 & 18 from text book

Q3 (a) Derive the relationship between transconductance and output conductance for MOS transistors.

Answer:

Transconductance expresses the relationship between o/p current I_{ds} and i/p voltage V_{gs} and is defined as

$$g_m = \frac{\delta I_{ds}}{\delta V_{gs}} \Big|_{V_{ds} = \text{constant}}$$

$$\text{Transit time } \tau = \frac{Q_c}{I_{ds}}$$

Thus change in current

$$\delta I_{ds} = \frac{\delta Q_c}{\tau}$$

$$\tau = \frac{L^2}{\mu V_{ds}}$$

$$\delta I_{ds} = \frac{\delta Q_c V_{ds} \mu}{L^2}$$

$$\delta Q_c = C_g \delta V_{gs}$$

$$\text{So that } \delta I_{ds} = \frac{C_g \delta V_{gs} \mu V_{ds}}{L^2}$$

$$\text{Now } g_m = \frac{\delta I_{ds}}{\delta V_{gs}} = \frac{C_g \mu V_{ds}}{L^2}$$

$$\text{In saturation } V_{ds} = V_{gs} - V_{t}$$

$$g_m = \frac{C_g \mu}{L^2} (V_{gs} - V_t)$$

$$\text{Substitute for } C_g = \frac{\epsilon_{ins} \epsilon_0 W L}{D}$$

$$g_m = \frac{\mu \epsilon_{ins} \epsilon_0 W}{D L} (V_{gs} - V_t)$$

$$\text{or } g_m = \beta (V_{gs} - V_t)$$

$$\text{where } \beta = \frac{\mu \epsilon_{ins} \epsilon_0 W}{D \cdot L}$$

Q3 (b) Explain CMOS inverter.

Answer

6. CMOS Inverter :-

The current/voltage relationship for MOS Transistor

$$I_{ds} = k \frac{W}{L} (V_{gs} - V_t) V_{ds} - \frac{V_{ds}^2}{2}$$

in the resistive region

$$I_{ds} = k \frac{W}{L} (V_{gs} - V_t)^2 \quad \text{in saturation}$$

In both cases factor k is technology dependent parameter such that

$$k = \frac{\epsilon_{ins} \epsilon_0 \mu_n}{D}$$

The factor W/L is contributed by geometry and it is common



$$\beta = k \frac{W}{L}$$

so that $I_{ds} = \frac{\beta}{2} (V_{gs} - V_t)^2$

$$\beta_n = \frac{\epsilon_{ins} \epsilon_0 \mu_n}{D} \frac{W_n}{L_n}$$

$$\beta_p = \frac{\epsilon_{ins} \epsilon_0 \mu_p}{D} \frac{W_p}{L_p}$$

 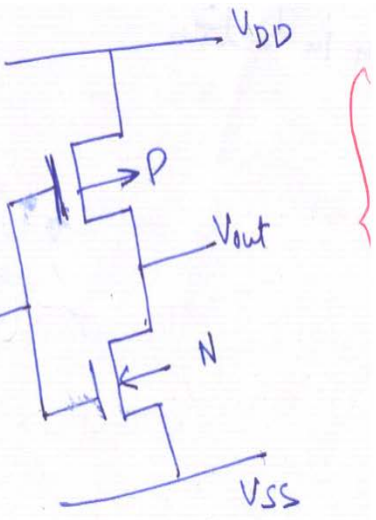Where W_n & L_n and W_p & L_p are n and p transistor dimensions respectively.



Q3 (c) Explain Bi CMOS Latch up susceptibility.

Answer

BiCMOS Latch-up Susceptibility:-

The benefit of the BiCMOS process is that it produces circuits which are less likely to suffer from latch up problem. This is due to several factors

- A reduction of substrate resistance
- A reduction of nwell resistance
- A reduction of R_s & R_w means that a larger lateral current is necessary to initiate latch up and a higher value of holding current is also required.
- The parasitic pnp transistors which is part of the nwell latch up circuit has its beta reduced owing to the presence of the buried n+ layer. This has the effect of reducing carrier lifetime in the n base region and this contributes the reduction in beta.

Q4 (a) Explain contact cuts in NMOS circuits.

Answer

4. Contact cuts in NMOS:- When contacts between polysilicon and diffusion in NMOS are made, there are three possible approaches (4)

1. Poly. to metal then metal to diff
2. a Buried contact poly. to diff.
3. a butting contact (poly to diff.)

When making connections between metal and either of other two layers the process is quite simple. The $2 \times 2 \times 2 \mu$ contact cut indicates an area in which the oxide is to be removed down to the ~~metal~~ underlying polysilicon or diffusion surface. When deposition of the metal layer takes place the metal is deposited through the contact cut areas onto the underlying area so that contact is made between the layers.

Fig. 3.8 and 3.9 : See Page 69 : Basic VLSI design
Douglas A. Pucknell

-67

Q4 (b) Write down the double metal MOS process rules.

Answer

- b. Double metal MOS Process Rules:-
1. Use the second level metal for global distribution of power buses (i.e. VDD and GND (VSS)) and for clock lines.
 2. Use the first level metal for local distribution of power and for signal lines.
 3. Lay out the two metal layers so that the conductors are mutually orthogonal wherever possible.


Q4 (c) Explain design rules for wires in 2µm CMOS.

Answer Page numbers 77 from text book

Q5 (a) Calculate the rise time and fall time of a CMOS inverter.

Answer

Rise Time Estimation:

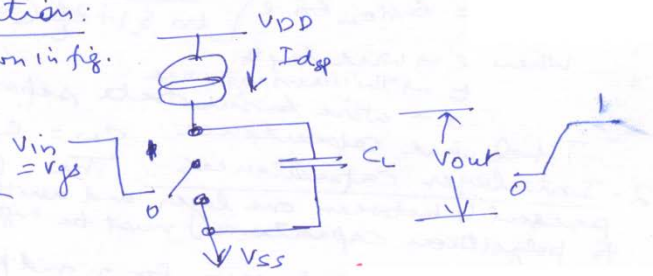The rise time model is shown in fig. 

CL is load capacitor

The saturation current for p-mos transistor is

$$I_{dsp} = \frac{\beta_p (V_{gs} - |V_{tp}|)^2}{2}$$

$$V_{out} = \frac{I_{dsp} t}{C_L}$$

$$t = \frac{2 C_L V_{out}}{\beta_p (V_{gs} - |V_{tp}|)^2}$$


for $t = t_r$ when $V_{out} = +V_{DD}$ so that

$$t_r = \frac{2 V_{DD} C_L}{\beta_p (V_{DD} - |V_{tp}|)^2}$$

If $|V_{tp}| = 0.2 V_{DD}$, then

$$t_r = \frac{3 C_L}{\beta_p V_{DD}}$$

Fall time Estimation:-

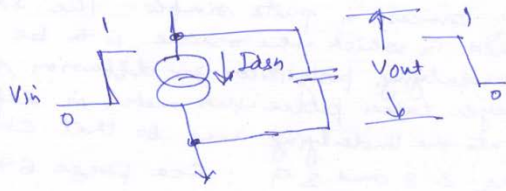Discharge is through n-mos transistor. The circuit model is shown in fig. 

$$t_f = \frac{3 C_L}{\beta_n V_{DD}}$$

Q5 (b) Explain the sources of capacitance which contribute to the overall wiring capacitance.

Answer:

6. There are three sources which contribute to wiring capacitance

1. Fringing Fields
2. Interlayer Capacitances
3. Peripheral Capacitances.

1. Fringing Fields: → The capacitance due to fringing field effects is ~~major~~ components of the overall capacitance of interconnect wires.

$$C_{ff} = \epsilon_0 \epsilon_{r2} \epsilon_0 l \left\{ \frac{\pi}{\ln \left\{ 1 + \frac{2d}{t} \left(1 + \sqrt{1 + \frac{t}{2d}} \right) \right\}} \right\} - \frac{t}{4d}$$

When $l \rightarrow$ wire length

$t \rightarrow$ thickness of wire

$d \rightarrow$ wire to substrate separation

2. Interlayer Capacitances: $C_w = C_{area} + C_{ff}$
The parallel plate effects are present between one layer and another. For a given area, the metal to polysilicon capacitance must be higher than metal to substrate.

3. Peripheral Capacitance: - For n and p regions formed by a diffusion regions are formed by impurity implant at the surface of silicon. These become important as we shrink the device dimensions.

$$C_{total} = C_{area} + C_{periph}$$

Q6 (a) Derive an expression for depletion width.

Answer:

Q Depletion width:- As channel length of MOS transistor is reduced, the depletion region widths must also be scaled down to prevent the source and drain depletion regions from meeting. The depletion region width d for junctions

$$d = \sqrt{\frac{2 \epsilon_{si} \epsilon_0 V}{q N_B}}$$

where ϵ_{si} → relative permittivity of Si
 ϵ_0 → permittivity of free space
 V → effective voltage
 q → charge on electron
 N_B → doping level of substrate
 V_a → applied voltage
 V_B → built-in potential

$$V_B = \frac{kT}{q} \ln\left(\frac{N_B N_D}{n_i^2}\right)$$

N_D → source or drain doping
 n_i → intrinsic carrier concentration in Si.

$$E_{max} = \frac{2V}{d}$$

When N_B is increased by d and if $V_a = 0$, then V_B is increased by $\ln d$ and d is decreased by $\sqrt{\frac{\ln d}{2}}$ for $E_{max} = E_{crit}$.

$$d = \sqrt{\frac{2 \epsilon_{si} \epsilon_0 \left(\frac{E_{crit} \cdot d}{2}\right)}{q N_B}}$$

or
$$d = \frac{\epsilon_{si} \epsilon_0 E_{crit}}{q N_B}$$

Q6 (b) Explain the structured design of multiplexer.

Answer:

Structured Design of Multiplexer: - Multiplexers are widely used and have many applications. Consider a four-way multiplexer. The requirements and general arrangement for a 4-way multiplexer are set out in fig. and we may write

$$Z = I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0$$

$S_0, S_1 \rightarrow$ Select Inputs
logic

The implementation is shown below

S_1	S_0	Z
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(AND gates)


Q7 (a) Where the various approaches used at different stages of VLSI design process? Explain the basic architecture of 4 bit digital processor.

Answer:

Approaches at different stages of VLSI design process

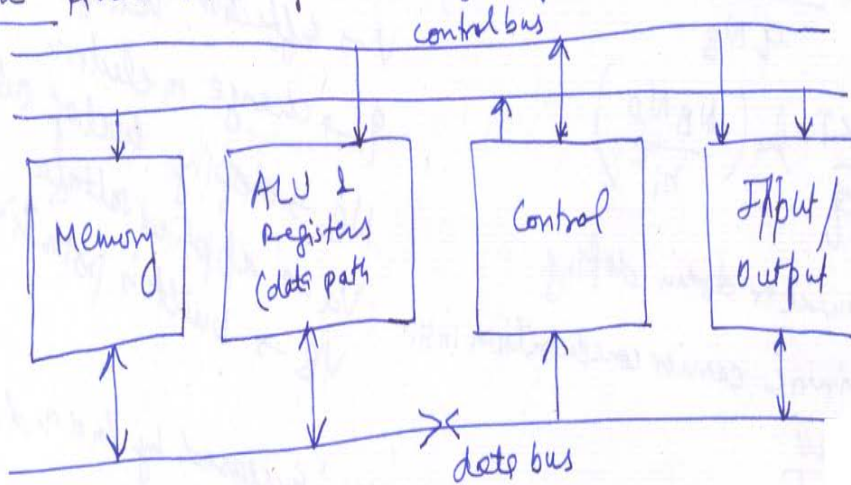1. Conventional ~~logic~~ circuit symbols
2. Logic symbols
3. Stick diagram
4. Any mixture of logic symbols
5. Mask layouts
6. Architectural block diagram
7. floor plans.

Basic Architecture of 4-bit digital processor



(Basic digital processor structure)


The data path is ~~seen~~ that the structure comprises a unit which processes data applied at one port and presents its output at a second port. Two data paths may be combined a single bidirectional port if storage facilities exists in the path. Control over the functions to be performed is effected by control signals as indicated.

We decompose the data path into blocks showing main subunit. It is useful to anticipate a possible floor plan to show the planned relative disposition of subunits on the chip and thus on the mask layouts.

 
Q7 (b) Design a 4 bit adder.

Answer:

of summands
 b. Design of 4-bit Adder:- In order to design the requirements for n bit add, consider the addition of two binary nos A and B.



 For any column k, there will be three inputs, corresponding bits and previous carry (C_{k-1}). There are two outputs, the sum S_k and carry C_k.



Inputs			O/Ps	
A _k	B _k	C _{k-1}	Sum	New carry C _k
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	1
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

$$S_k = H_k \bar{C}_{k-1} + \bar{H}_k C_{k-1} \quad \text{--- (1)}$$

where $H_k = \bar{A}_k B_k + A_k \bar{B}_k$
 $H_k \rightarrow$ Half Sum

$$\text{New Carry } C_k = A_k B_k + H_k C_{k-1} \quad \text{--- (2)}$$

These equations are directly implemented as AND-OR functions.

Truth table

Q8 (a) What are the factors considered to make a comparative assessment of the dynamic shift registers?

Answer:

Factors considered to make comparative assessment for the dynamic shift register. (6)

1. Area requirement
2. Estimated dissipation
3. Validity

1. Area: Consider the case of NMOS design with buried contacts. Allow for sharing of V_{DD} and GND rails between adjacent rows of register cells. The each bit stored will require $22\lambda \times 28\lambda = 1200\lambda^2$
 for $\lambda = 2.5 \mu m$, Area per bit = $7500 \mu m^2$

For CMOS $(38\lambda \times 28\lambda) \times 2 = 400\lambda^2$
 $\lambda = 2.5 \mu m$ Area per bit = $13000 \mu m^2$

2. Dissipation: In case of CMOS static dissipation is very small, the dynamic power consumption $P_d = m C_L V_{DD}^2 f$

Where $m \rightarrow$ duty cycle

$C_L \rightarrow$ effective load capacitance

$f \rightarrow$ clock frequency.

In NMOS, $2p_u = 4R_s$

and $2p_d = \frac{1}{2} R_s$

$C_{current} = \frac{V_{DD}}{2p_u + 2p_d} \Rightarrow \frac{\text{The static dissipation}}{\text{Bit stored}} = \frac{V_{DD} \times C_{current}}{\text{Bit stored}}$

3. Validity: Data is stored by the charge on the gate capacitor of each inverter stage so that data storage time is limited to 1 μ sec or less.

Q8 (b) Explain floor plan layout of a 4-bit processor.

Answer:

inverted sig

b. The floor plan of 4 bit processor: The basic floor plan is shown in Fig 11.1. There are three main subsystems and determined boundary boxes with interconnection dispositions in the complete system. The dominant feature of the layout being interspersing of the address and data having already redesigned to allow stretching to match the address.

has 2 I/O control, register select and control and ALU control.
 Bus A connects I/O ports to register array and carries operand.
 Bus B connects register array with other I/P. B is bidirectional.

Q9 Write short note on:

- (i) Design Rule Checkers
- (ii) CIF code
- (iii) CAD Tools for design and simulation
- (iv) Signature Analysis in BIST

Answer:

(i) Design Rule Checkers: - The cost in time and facility in mask-making and fabricating a chip from those masks is such that all possible errors must be eliminated before checking proceeds. Once a design has been turned into silicon there is little that can be done to check for errors at all stages of design, namely:

1. At the pencil and paper stage of design of leaf-cells.
2. At the leaf-cell level once the layout is complete.
3. At subsystem level to check that putting together and wiring up the leaf-cells is correctly done.
4. Once the entire system layout has been completed.

The nature of physical layout verification design rule checking software depend on whether the design rules are absolute or λ based or on whether or not the layout is on a fixed or virtual grid.

(ii) Answer: Page numbers 293 from text book

(iii) Answer:

(ii) CAD Tools for Design and Simulation: - The design of a chip of reasonable complexity can in time be completed by hand, but it is both a hard and inefficient way of doing things. As far as the design of systems is concerned, it is essential to have computer aids to design so that the design can be completed in a reasonable time. The designer tools should include


1. Physical design layout and editing capabilities.
2. Structure generation / system composition capabilities.
3. Physical verification: It includes design rule checking, circuit extractors, ratio rule and other static checks and a capability to plot out and/or display for visual checking.
4. Behavioural verification: Simulation at various levels will be required to check out the design before one embarks on the expense of turning out the design in silicon.

(iv) Answer:

IV) Signature Analysis In BIST

BIST stands for Built-In Self Test. The BIST techniques aim to effectively integrate automatic test system into the chip design. The test compacting scheme currently used most is called signature analysis. It performs polynomial division that is to say division of the data out of the device under test. This data is represented as a polynomial $P(x)$ which is divided by a characteristic polynomial $C(x)$ to give signature $R(x)$ so that

$$R(x) = P(x) / C(x)$$

 

The signature for DUT is compared with the expected signature to determine if the DUT is fault free. The difference between the faulty signature and a good signature may also be used to indicate the nature of the fault. Signature analysis has been proved to be a reliable and attractive alternative to full uncompact testing.

Text Book

Basic VLSI Design, Douglas A. Pucknell & Kamran Eshraghian, PHI, 3rd Edition, 2007