

**Q2 (a) Describe the four methods available for fabricating Integrated Resistors and explain Thin Film Resistor with a neat sketch.**

**Answer** Refer to page numbers 22 & 25 from text book II

**Q2 (b) Explain Complementary MOSFET fabrication process with neat sketch.**

**Answer** Refer to page numbers 30 from text book II

**Q3 (a) Draw the h-parameter equivalent circuit of Common Emitter Amplifier circuit and derive the expression for input impedance, output impedance, voltage gain and current gain.**

**Answer** Refer to page numbers 254 & 258 from text book I

**Q3 (b) Compare CE, CB and CC. Discuss typical application of each.**

**Answer**

(b) **Solution to the Numerical:**

Given data:  $I_B = 20 \mu A$  and  $I_C = 1 \text{ mA}$

The AC resistance for transistor BE junction,  $r_e' = \frac{26mV}{I_E} \approx \frac{26mV}{1mA} = 26\Omega$

The current gain,  $\beta = h_{fe} \approx \frac{I_C}{I_B} \approx \frac{1mA}{20\mu A} = 50.$

The input resistance,  $r_\pi = h_{ie} = (1 + h_{fe})r_e' = (1 + 50) \times 26\Omega$   
 $\approx 1.33K\Omega$

**Q4 (a) Sketch a typical drain characteristic for  $V_{GS} = 0$  for an N-channel JFET. Explain the shape of the characteristic and identify the regions.**

**Answer** Refer to page numbers 350 & 351 from text book I

**Q4 (b) An N-channel JFET has drain-source saturation current ( $I_{DSS}$ ) = 8.7 mA, pinch-off voltage ( $V_P$ ) = - 3V and gate-source voltage ( $V_{GS}$ ) = -1 V. Determine:**

- (i) Drain current ( $I_D$ )
- (ii) Transconductance for  $V_{GS} = 0$  ( $g_{mo}$ )
- (iii) Transconductance ( $g_m$ )

**Answer****(b) Solution to the Numerical:**

Given data: Drain-source saturation current,  $I_{DSS} = 8.7\text{mA} = 0.0087\text{A}$

Pinch-off voltage,  $V_P = -3\text{V}$

Gate-source voltage,  $V_{GS} = -1\text{V}$

$$(i) \text{ Drain current, } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 0.0087 \left(1 - \frac{-1}{-3}\right)^2$$

$$I_D = 3.8667\text{mA}$$

(ii) Transconductance for  $V_{GS} = 0$ ,

$$g_{mo} = \frac{-2I_{DSS}}{V_P} = \frac{-2 \times 8.7\text{mA}}{-3} = 5.8\text{mA/V or } 5.8\text{mS}$$

(iii) Transconductance,

$$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_P}\right) = 5.8 \left(1 - \frac{-1}{-3}\right) = 3.867\text{mA/V or } 3.867\text{mS}$$

**Q5 (a) Explain with a diagram, the working of a transformer coupled class AB power amplifier.**

**Answer** Refer to page numbers 818 & 819 from text book I

**Q5 (b) What is an Opto-coupler? Explain its construction and operation with neat diagrams.**

**Answer** Refer to page numbers 971 & 972 from text book I

**Q6 (a) Draw the block diagram of Op-Amp internal circuit and explain the function of each block briefly.**

**Answer** Refer to page numbers 53 from text book II

**Q6 (b) Derive an expression for the voltage gain of Non-Inverting Op-Amp.**

**Answer** Refer to page numbers 47 & 48 from text book II

**Q6 (c) What are the various DC characteristics of Op-Amp? Explain Input Offset Voltage.**

**Answer** Refer to page numbers 104, 108 & 109 from text book II

**Q7 (a) Draw the circuit diagram of Sample and Hold circuit using op-amp and explain its operation with the help of input and output waveforms.**

**Answer** Refer to page numbers 153 & 154 from text book II

**Q7 (b) Explain the working of integrator using Op-Amp**

**Answer** Refer to page numbers 168 & 169 from text book II

**Q8 (a) Draw the circuit diagram of triangular waveform generator using op-amp and describe its operation with waveforms.**

**Answer** Refer to page numbers 220 & 222 from text book II

**Q8 (b) Draw the circuit of monostable multivibrator using 555 timer and explain its operation.**

**Answer** Refer to page numbers 312 & 314 from text book II

**Q9 (a) Draw the functional block diagram of 723 general purpose voltage regulator IC and explain its operation.**

**Answer** Refer to page numbers 248 & 250 from text book II

**Q9 (b) Draw the block diagram of Counter Type A/D Converter and explain its operation with the help of waveform**

**Answer** Refer to page numbers 360 & 361 from text book II

### Text Book

**Text book I: Electronic Devices and Circuits by David A. Bell 4th Edition, Ph (2006).**

**Text book II: Linear Integrated Circuits by D .Roy Choudhry and Shail B. Jain , New Age International Publishers, revised 2 nd Edition .**